

Combinational Logic II

CS207 Lecture 6

James YU


Mar. 25, 2020



南方科技大学
SOUTHERN UNIVERSITY OF SCIENCE AND TECHNOLOGY


Decoder

 - The basic function of an MSI decoder having n inputs is to select 1-out-of- 2^n output lines.
 - The selected output is identified either by a 1, when all other outputs are 0, or by a 0 when all other outputs are 1.




Decoder

 - It will be seen that the logic diagram of the basic decoder is identical to that of the basic demultiplexer.
 - Provided the data line is used to enable the decoder.
- The decoder may also be regarded as a minterm generator. Each output generates one minterm.



Decoder

 
- If $A = B = C = D = 0$ the output 0 of the decoder is active low while all other outputs are 1.
- The decoder can generate the inverse of the 16 minterms.
- Example: $f(A, B, C, D) = \sum(0, 1, 5, 8, 10, 12, 13, 15)$.



Decoder network


- When a large decoding network is required it cannot be implemented in a single MSI package.
 - Mainly because of the large number of pins needed.
- The decoding range can be extended by interconnecting decoder chips. Two schemes:
 - *Tree decoding.*
 - *Coincident decoding.*

Decoder network

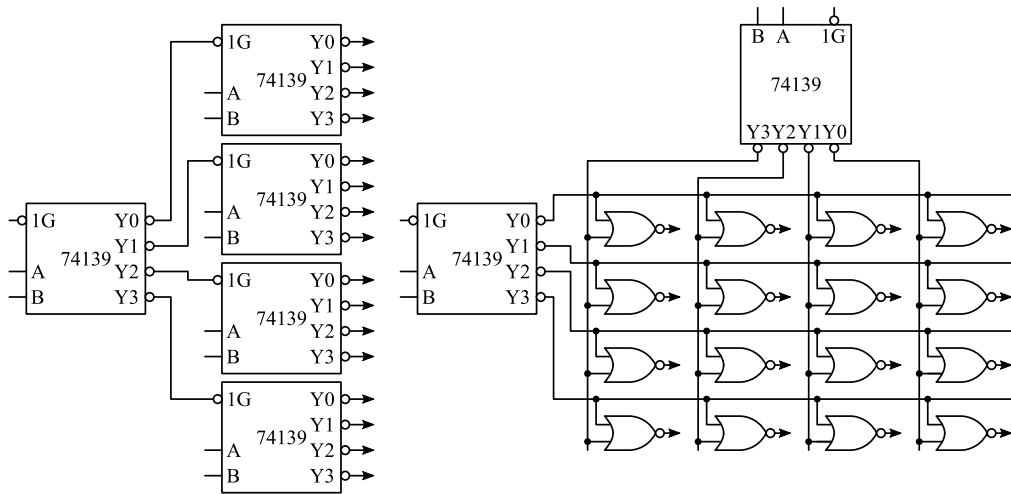

Encoder

 - An encoder performs the inverse operation to that of a decoder.
- Example: CPU master flag



- The encoder is designed to identify one, and only one, of the peripherals at any given instant.
 - In practice, there is nothing to prevent two or more peripherals requesting service at the same time.
 - To deal with this situation a system of priorities can be attached to the peripheral flags.



Encoder

- Example: Octal-to-binary encoder.

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- Eight inputs and three outputs connected with OR.



Encoder

- $x = D_4 + D_5 + D_6 + D_7$.
- $y = D_2 + D_3 + D_6 + D_7$.
- $z = D_1 + D_3 + D_5 + D_7$.
- Only one input can be active for one time.
 - D_3 and D_6 are 1 simultaneously: outputs $(111)_2 = 7$.
 - Encoder circuit must have priority: *Priority encoder*.

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	x	x	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1



Encoder

$$x = D_2 + D_3$$

		D_2D_3			
		00	01	11	10
D_0D_1	00	X	1	1	1
	01	0	1	1	1
	11	0	1	1	1
	10	0	1	1	X


$$y = D_3 + D_1D_2'$$

		D_2D_3			
		00	01	11	10
D_0D_1	00	X	1	1	0
	01	1	1	1	0
	11	1	1	1	0
	10	0	1	1	0



Encoder

 - $x = D_2 + D_3$.
- $y = D_3 + D_1 D_2'$.
- $V = D_0 + D_1 + D_2 + D_3$.




Digital comparator

- The usual problem for a comparator is the comparison of two multi-digit words such as $A = A_2A_1A_0$ and $B = B_2B_1B_0$.
 - Start from most to least significant bit.
 - $A = B$ if all bits are equal: $A_i = B_i$.
 - $x_i = A_iB_i + A'_iB'_i$.
- $A = B$ if $x_2x_1x_0 = 1$.
- $A > B$ if $A_2B'_2 + x_2A_2B'_2 + x_2x_1A_0B'_0 = 1$.
- $A > B$ if $A'_2B_2 + x_2A'_2B_2 + x_2x_1A'_0B_0 = 1$.



Digital comparator

 
- The implementation of a 3-bit comparator is based on a single bit comparator.



- Using the equations developed in the last page, we can have a 3-bit comparator.



Digital comparator

 

Verilog: Task

- Tasks are used in all programming languages, generally known as procedures or subroutines.
- The lines of code are enclosed in `task...end` task brackets.
- Data is passed to the task, the processing done, and the result returned.
- They have to be specifically called, with data `ins` and `outs`, rather than just wired in to the general netlist.
- Included in the main body of code, they can be called many times, reducing code repetition.
- Tasks are defined in the module in which they are used.
 - It is possible to define a task in a separate file and use the compile directive `'include` to include the task in the file which instantiates the task.

Verilog: Task

- A task begins with keyword `task` and ends with keyword `endtask`.
- Inputs and outputs are declared after the keyword `task`.
- Local variables are declared after input and output declaration.

```
1 module simple_task();  
2 task convert;  
3 input [7:0] temp_in;  
4 output [7:0] temp_out;  
5 begin  
6     temp_out = (9/5) *(temp_in + 32)  
7 end  
8 endtask  
9 endmodule
```



Verilog: Task

```
1 module task_calling (temp_a, temp_b, temp_c, temp_d);
2   input [7:0] temp_a, temp_c;
3   output [7:0] temp_b, temp_d;
4   reg [7:0] temp_b, temp_d;
5   `include "mytask.v"
6
7   always @ (temp_a)
8   begin
9     convert (temp_a, temp_b);
10  end
11  always @ (temp_c)
12  begin
13    convert (temp_c, temp_d);
14  end
15 endmodule
```



Verilog: Function

- A Verilog **function** is the same as a task, with very little differences, like **function** cannot drive more than one output, can not contain delays.
 - Functions can not include timing delays, like **posedge**, **negedge**, **#** delay, which means that functions should be executed in “zero” time delay.
 - Functions can have any number of inputs but only one output.
 - Functions can call other **functions**, but can not call **tasks**.

```
1 module simple_function();  
2 function myfunction;  
3 input a, b, c, d;  
4 begin  
5     myfunction = ((a+b) + (c-d));  
6 end  
7 endfunction  
8 endmodule
```



Verilog: Function

```
1 module function_calling(a, b, c, d, e, f);  
2   input a, b, c, d, e;  
3   output f;  
4   wire f;  
5   `include "myfunction.v"  
6  
7   assign f = (myfunction (a,b,c,d)) ? e : 0;  
8 endmodule
```



Verilog: Operators

- In Verilog, operators can be classified into multiple categories, i.e., arithmetic, relational, equality, logical, bit-wise, reduction, shift, concatenation, replication, and conditional operators.
- **Arithmetic operators:**
 - $+$, $-$, $*$, $/$ — binary modulus operator.
 - $+$, $-$ — unary operator used to specify the sign.
 - Integer division truncates any fractional part.
 - If any operand bit value is the unknown value x , then the entire result value is x .



Verilog: Operators

- **Relational operators:**

- $a < b$ — a less than b.
- $a > b$ — a greater than b.
- $a \leq b$ — a less than or equal to b.
- $a \geq b$ — a greater than or equal to b.
- The result is a scalar value (example $a < b$).
 - 0 if the relation is false (a is bigger than b).
 - 1 if the relation is true (a is smaller than b).
 - x if any of the operands has unknown x bits (if a or b contains x).



Verilog: Operators

- **Equality operators:**

- $a === b$ — a equal to b , including x and z (Case equality).
 - $a !== b$ — a not equal to b , including x and z (Case inequality).
 - $a == b$ — a equal to b , result may be unknown (logical equality).
 - $a != b$ — a not equal to b , result may be unknown (logical equality).
- Operands are compared bit by bit, with zero filling if the two operands do not have the same length.
 - For the $==$ and $!=$ operators, the result is x , if either operand contains an x or a z (high impedance, or open circuit).
 - For the $===$ and $!==$ operators, bits with x and z are included in the comparison and must match for the result to be true.



Verilog: Operators

- **Logical operators:**
 - `!` — logic negation.
 - `&&` — logical and.
 - `||` — logical or.
- Expressions connected by `&&` and `||` are evaluated from left to right.
- Evaluation stops as soon as the result is known.
- The result is a scalar value:
 - `0` if the relation is false.
 - `1` if the relation is true.
 - `x` if any of the operands has `x` (unknown) bits.



Verilog: Operators

- **Bit-wise operators:**
 - \sim — negation.
 - $\&$ — and.
 - $|$ — inclusive or.
 - \wedge — exclusive or.
 - $\wedge\sim$ or $\sim\wedge$ — exclusive nor (equivalence).
- When operands are of unequal bit length, the shorter operand is zero-filled in the most significant bit positions.

Verilog: Operators

- **Concatenations** are expressed using the brace characters { and }, with commas separating the expressions within.

- Example:

```
1 {a, b[3:0], c, 4'b1001} // if a and c are 8-bit numbers,  
    the results has 24 bits.
```

- Un-sized constant numbers are not allowed in concatenations.
- **Replication** operator is used to replicate a group of bits n times.
 - Say you have a 4 bit variable and you want to replicate it 4 times to get a 16 bit variable: then we can use the replication operator.

```
1 {3{a}} // this is equivalent to {a, a, a}  
2 {b, {3{c, d}} } // this is equivalent to {b, c, d, c, d, c,  
    d}
```



Verilog: Operators

- The `conditional operator` has the following Java-like format: `cond_expr ? true_expr : false_expr`.
- The `true_expr` or the `false_expr` is evaluated and used as a result depending on what `cond_expr` evaluates to (`true` or `false`).