# **Computer Organization**


Lab9 CPU Design1: Decoder and DataMemory

2021 Spring term wangw6@sustech.edu.cn

### **Topics**

- CPU Design(1)
  - ISA
  - Data Path(1)
    - Decoder
    - Data Memory
      - Customize block memory IP core
      - Instance IP core to build Data Memory

### ISA-MIPS

 

#### BASIC INSTRUCTION FORMATS

R	opco	de	rs	rt	rd	sha	mt	funct
	31	26 25	21	20	16 15	11 10	6 5	0
	opco	de	rs	rt		imm	ediate	(Funct?)
	31	26 25	21	20	16 15			(
	opcode				addre	ldress		
	31	26 25						(

### MIPS addressing


- 1. immediate addressing:
  - addi \$s0,\$s1,5 (1)
- 2. register addressing:
- 3. base addressing:
  - lw \$s0,0 (\$s1) 【I】
- 4. pc-relative addressing
  - bne \$s0,\$s1,EXIT [I]
- 5. psudo-directive addressing
  - j EXIT 【J】

### **How CPU works**

- Fetch the instruction from the instruction memory according to the value of the PC register
- Analyze the instruction to get how to process the data
- Execute the instruction
  - R type:
    - [add]: find the register and read its value, do the arithmetic calculation, write the register
  - I type:
    - [addi]: same as add except one of operands is from the immediate number of the instruction
    - [branch]: find the register and read its value, do the comparation and write the PC register with the target address(pc relative addressing)
    - [load/store]: find source data from the register/memory, read its value to wirte the targert place
  - J type:
    - [j]: write the PC register with the target address(presdo-directory addressing)
    - [ir]: write the PC register with the value of \$31
    - [jal]: write \$31 and the PC register


### **Core Modules in CPU**

reference from Minisys, a

 

### Decoder



 

- There are 32 registers in the decoder, each register is 32bits width
- All the registers are readable and writeable except \$0, \$0 is readonly.
- The read should be done at any time while write only happens on the bosedge of the clock.
- The register file should support R/I/J type instructions.
  - such as: add, addi, lw, sw, jal, jr




opcode, function code: how to get data, where to get data

immediate data in the instruction([15:0]), (e.g. immi = Instruction[15:0]) need to be signextended to 32bits (版图 167b拼播


- data in the register, the address of the register is coded in the instruction. e.g. rs = Instruction[25:21];
- data in the memory, the address of the memory unit need to be calculated by ALU with base address stored in the register and offset as immediate data in the instruction
- Read/Write data from/to Register File

#### BASIC INSTRUCTION FORMATS

R	opco	ode	rs	rt	rd	shamt	funct
	31	26 25	21 20	16	15 1	1 10 6	5 0
I	opco	de	rs	rt		immediat	e
	31	26 25	21 20	16	15		0
I	opcode				address		
	31	26 25					0

 

### **Decoder** continued

 

- 1. Create the decoder as specified on page 6~7
- There are 32 reaisters in the decoder, each reaister is 32bits width
- All the registers are readable and writeable except \$0, \$0 is readonly.
- The read should be done at any time while write only happens on the posedge of the clock.
- The register file should support R/I/J type instructions.
  - such as: add, addi, lw, sw, jal, jr

#### Register File

#### Inputs

- read address
  - [R] add: rs,rt
    - [J] jr: [31]
- write address
  - [R] add: rd
  - [J] jal : [31]
  - [I] addi: rt
- write data
  - [R] add: alu\_result
  - [J] jal : pc+4
  - [I] load: data from memory
- control signal
  - [R] /[I]/[J] writeRegister
  - [J]: ja
  - [I]: memToReg
  - [R]/[I]: rd vs rt

#### BASIC INSTRUCTION FORMATS

R	opc	ode	rs	rt	1	rd	shamt	funct
	31	26 25	21 2	.0	16 15	11 1	10 65	(
I	opc	ode	rs	rt			immediate	
	31	26 25	21 2	0	16 15			(
J	opc	ode			ad	dress		
	31	26 25						(

- Register File
- Outputs
  - read data1
  - read data2
  - extendedlmmi


### Decoder continued

#### BASIC INSTRUCTION FORMATS rd shamt opcode rt 21.20 16 15 11 10 26 25 opcode rt immediate rs 26 25 21 20 16 15 address oncode 26 25
 
#### Register File:

Almost all the instructions need to read or write register file in CPU 32 common registers with same bitwidth: 32





//verilog tips: reg[31:0] register[0:31]; assign Read data 1 = register[Read register 1] register[Write register] <= WriteData;

### Q1:

How to avoid the confliction between register read and register write?

Q2: Which kind of circuit is this register file, combinatorial circuit or sequential circuit?

Q3: How to determine the size of address bus on register file?




### Practice1

- 1. Create the decoder as specified on page 6~7
  - There are **32** registers in the decoder, each register is **32bits** width
  - All the registers are readable and writeable except \$0, \$0 is readonly.
  - The read should be done at any time while write only happens on the posedge of the clock.
  - The register file should support R/I/J type instructions.
    - such as: add, addi, lw, sw, jal, jr
- 2. Verify its function by simulation.
- 3. List the signals which are used in the decoder

NOTE: Signals' name are determined by designer

name	from	to	bits	function
regWrite	instruction	decoder	1	1 means write the register identified by writeAdress
immediate	instruction	ALU	32	the signextended immediate
readRegister1	instruction	decoder	5	the address of read register instruction[25:21]

## Memory

 

module **dmemory32**(readData,address, writedata,memWrite,clock);

```
// Clock signal input clock;
```


// the address of memory unit which is tobe read/write input[31:0] address;

// used to determine to write or read input **memWrite**;

// data tobe wirte into the memory unit input[31:0] writeData;

// data tobe read from memory unit
output[31:0] readData;

## **Using IP core Block Memory**

 

Using the IP core Block Memory from Xilinx to implement the data memory.

Import the IP core in vivado project Step1:


in "PROJECT MANAGER" window click "IP Catalog"

### Step2:

in "IP Catalog" window

- > Vivado Repository
- > Memories & Storage Elements
- > RAMs & ROMs & BRAM
- > Block Memory Generator

## **Customize Memory IP core**

 


Using the IP core Block Memory from Xilinx to implement the data memory.

### customize memory IP core:

- Component Name: RAM
- Basic settings:
  - Interface Type: Native
  - Memory Type: Single-port RAM
  - ECC options: **no ECC check**
  - Algorithm options: Minimum area


## Customize Memory IP core continued

 
 
### Customize Memory IP core continued

- Other Options settings:
  - 1. When specifying the initialization file for RAM, the IP core RAM just customized WITHOUT initial file and corresponding path, so set it to no initial file when creating RAM.
  - 2. After creating the RAM
    - 2-1. copy the initialization file dmem32.coe to projectName.srcs/sources\_1/ip/RAM.
       ("projectName.srcs" is under the project folder)
    - 2-2. Double-click the newly created RAM IP core, reset it with an initialization file, select the dmem32.coe file that has been in the directory of projectName.srcs/sources\_1/ip/RAM.





### **Design Module With Memory IP Instanced**

```
BRAM PORTA
// Part of dmemory32 module
                                                                              ▶ addra[13:0]
//Generating a clk signal, which is the inverted clock of the clock signal
                                                                              ▶ dina[31:0]
assign clk = !clock;
                                                                              douta[31:0]
                                                                              ▶ weaf0:01
//Create a instance of RAM(IP core), binding the ports
RAM ram (
    .clka(clk),
                                    // input wire clka
    .wea(memWrite),
                                    // input wire [0 : 0] wea
    .addra(address[15:2]),
                              // input wire [13 : 0] addra
                              // input wire [31 : 0] dina
    .dina(writeData),
    .douta(readData)
                              // output wire [31:0] douta
);
```

**Notes:** Because the inherent delay of the chip is used, the address line of the RAM is not ready at the rising edge of the clock, which causes the data to be read incorrectly on the rising edge of the clock. Consider the method of using the inverted clock to make the read data more ready than the address. It takes about half a clock late to get the correct address.

### **Function Verification**

```
//The testbench module for dmemory32
module ramTb( );
reg clock = 1'b0;
reg memWrite = 1'b0;
reg [31:0] addr = 32'h0000 0010;
reg [31:0] writeData = 32'ha000 0000;
wire [31:0] readData;
dmemory32 uram
               (clock,memWrite,addr,writeData,readData);
always
    #50 \operatorname{clock} = \sim \operatorname{clock};
initial begin
  #200
     writeData = 32'ha0000 00f5;
     memWrite = 1'b1;
  #200
    memWrite = 1'b0;
end
endmodule
```

The "addr" is 0x0000\_0010

- 1) Set "memWrite" to low level and read the data of the address in RAM.
- 2) Set "memWrite" to high level and writeData to 0xa000\_00f5
- 3) Set "memWrite" to low level and read the data of the address in RAM.

17

000000000.

### Function Verification continued

```
memory initialization radix = 16;
memory initialization vector =
007f2812.
007f2811.
                                            Value
                      Name
007f2810.
                                                         0 ns | 200 ns | 400 ns | 600 ns |
007f2810.
                       6 addr[31:0]
                                           00000010
                                                                                           00000010
007f280f.
                       writeData[31:0]
                                          000000f5
                                                             a0000000
                                                                                                   0000d0f5
00000001.
00000002.
                       1 memWrite
00000003.
                       L clock
                                           0
00000005.
                       readData[31:0]
                                          000000f5
00000006.
                                                             007f280f
                                                                                                   0000d0f5
00000007.
0000ffff.
00000000.
```

Q1: On which edge of clock does the read and write operations occur? posedge or negedge?

Q2: What's value will be get while read the memory according to the "addr" 0x0000\_0016?

Tips: "dmem32.coe" file could be found in the directory "source/lab/lab9" of course sakai site <a href="https://sakai.sustech.edu.cn/portal/site/d50211ea-1586-4344-9d92-a6c42eb7f4e0/tool/b47e4c13-4220-4f61-b881-a211abee2a96?panel=Main">https://sakai.sustech.edu.cn/portal/site/d50211ea-1586-4344-9d92-a6c42eb7f4e0/tool/b47e4c13-4220-4f61-b881-a211abee2a96?panel=Main</a>

17=16+1

18 / Practice2

1. Build the data memory module following the steps list on page 11~15

NOTE: Using the same "dmem32.coe" as page 17 to initialize the memory ip core


- 2. Verify its function by simulation
  - Change the testbench by adding more testing
    - Read the values one by one from memory unit where are specified in the red box of the screenshot on the right hand.
    - Write a word(value is 0x1000\_0000) to the memory unit where is specified in the blue box of the screeshot on the left hand, then read it out.

3. List of the signals which are needed for data memory module

ore 8	8 9 10 11 12 13 14 15	00000001, 00000002, 00000003, 00000005, 00000006, 00000007, 0000ffff,	read these initial value
of Je	16 17 18 19 20 21	00000000, 00000000, 00000000, 00000000, 000000	write this word with 0x1000_0000 then read it
with	n its	negedg	le

memory\_initialization\_radix = 16;
memory\_initialization\_vector =

	name	from	to	bits	function
/	clock		Data Memory	1	memory write is sensitive with its negedge
	rdata	Data Memory	Decoder	32	the word read from the data memory and send to decoder
	Address	ALU Result	Dorta Memory	32	according to the address to read or write data
1	wdotta Tips: "dme	Decoler m32.coe" file could b	Data Memory De found in the directory	344-9d9	the word read from register and write to data memory.  (lab/lab9" of course sakai site  22-06642eb7f4e0/too//b47e4613-4220-4f61-b881-0211gbee20968panel=Main

 

**Control Path**: Interprete instructions and generate signals to control the data path to execute instructions

**Data Path**: The parts in CPU with componets which are involved to execute instructions