

A decorative graphic on the left side of the slide, consisting of a network of white lines and small circles on a blue gradient background, resembling a circuit board or a tree structure.


DIGITAL DESIGN

LAB11 FSM MOORE MEALY

2020 FALL TERM @ CSE . SUSTECH


COMBINATORIAL VS SEQUENTIAL
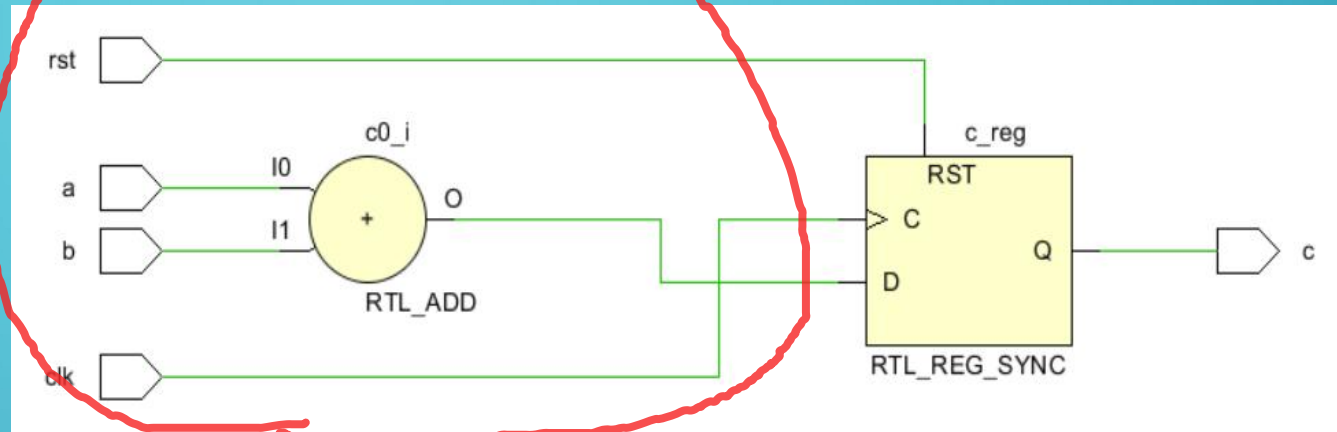
```
`timescale 1ns / 1ps
//
module s_adder(input clk,rst,a,b, output c );
  reg c;
  always @(posedge clk)
  begin
    if(rst)
      c<=0;
    else
      c<=a+b;
  end
end
endmodule
```



```
module test_assign(input a,clk,output y1,y2 );
  reg b,c,y1,y2;
  always @ *
  begin
    b=a;
    y1=b;
  end

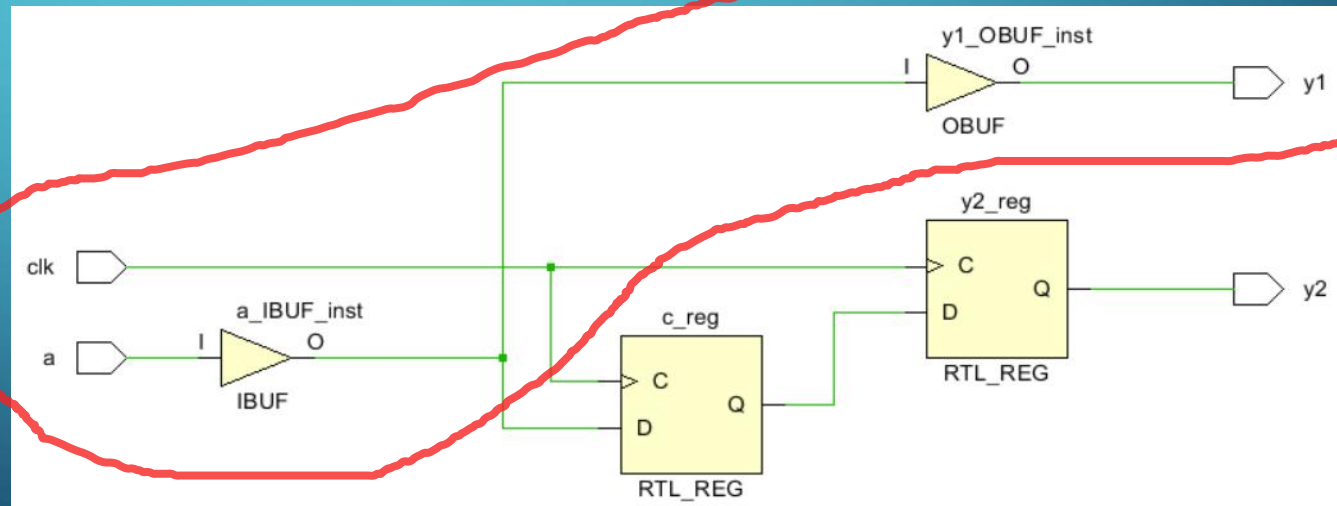  always @(posedge clk)
  begin
    c<=a;
    y2<=c;
  end
end
endmodule
```



Strongly recommend: using blocking-assignment in combinational circuit while using non-blocking-assignment in sequential circuit


FSM : FINITE STATE MACHINES

An FSM is defined by a list of its states, its initial state, and the conditions for each transition. Finite state machines are of two types – deterministic finite state machines and non-deterministic finite state machines.^[1] A deterministic finite-state machine can be constructed equivalent to any non-deterministic one.

When describing a FSM, the key is to clearly describe several elements of the state machine :

- how to make state transition
- the conditions of state transition
- what is the output of each state.

 Generally speaking, the state transition part is a synchronous sequential circuit after the state machine is implemented, and the judgment of the state transition condition is combinational logic.





3 WAYS ON FSM

- (1) **One-stage:** The whole FSM is written into an always block, which describes not only the state transition, but also the input and output of the state. (NOT suggested)
- (2) **Two-stages:** two always blocks are used to describe the state machine, one of which uses synchronous time series to describe the state transition; the other uses combinational logic to judge the condition of state transition, to describe the law of state transition and output;
- (3) **Three-stages:** One always module uses synchronous timing to describe state transition, One always uses combination logic to judge state transition conditions and describe state transition rules, and the Other always block describes state output (which can either be output of combination circuit or the output of sequential circuit).

Generally speaking, the recommended FSM description method is the latter two. This is because: FSM, like other designs, is best designed in a synchronous sequential manner to improve the stability of the design and eliminate burrs.

MOORE MODE

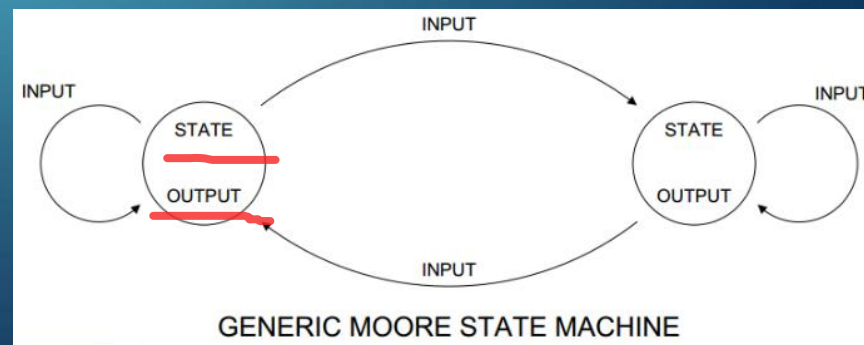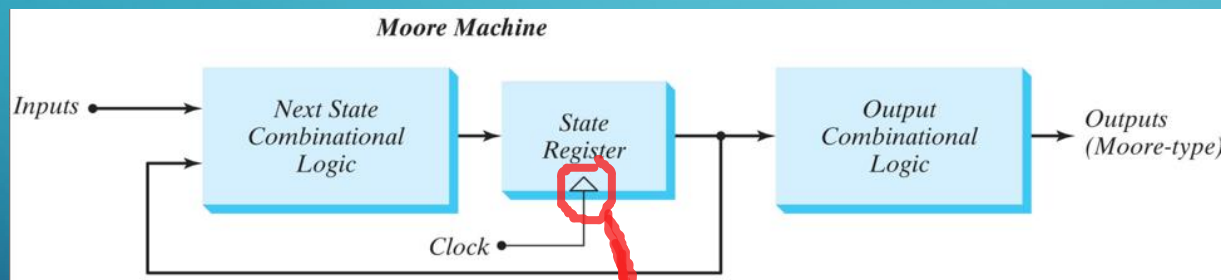
- Outputs are functions of present state only
- Outputs are synchronized with clock



output和state直接相关


MOORE MODE WITH 1 STAGE

```
`timescale 1ns / 1ps
//////////////////////////////////////////////////
module moore_1b(input clk,rst_n,x_in,output[1:0] state);
  reg [1:0] state;
  parameter S0=2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
  always @(posedge clk,negedge rst_n) begin
    if(~rst_n)
      state <= S0;
    else
      case(state)
        S0: if(x_in) state <= S1; else state <= S0;
        S1: if(x_in) state <= S2; else state <= S1;
        S2: if(x_in) state <= S3; else state <= S2;
        S3: if(x_in) state <= S0; else state <= S3;
      endcase
  end
endmodule
```

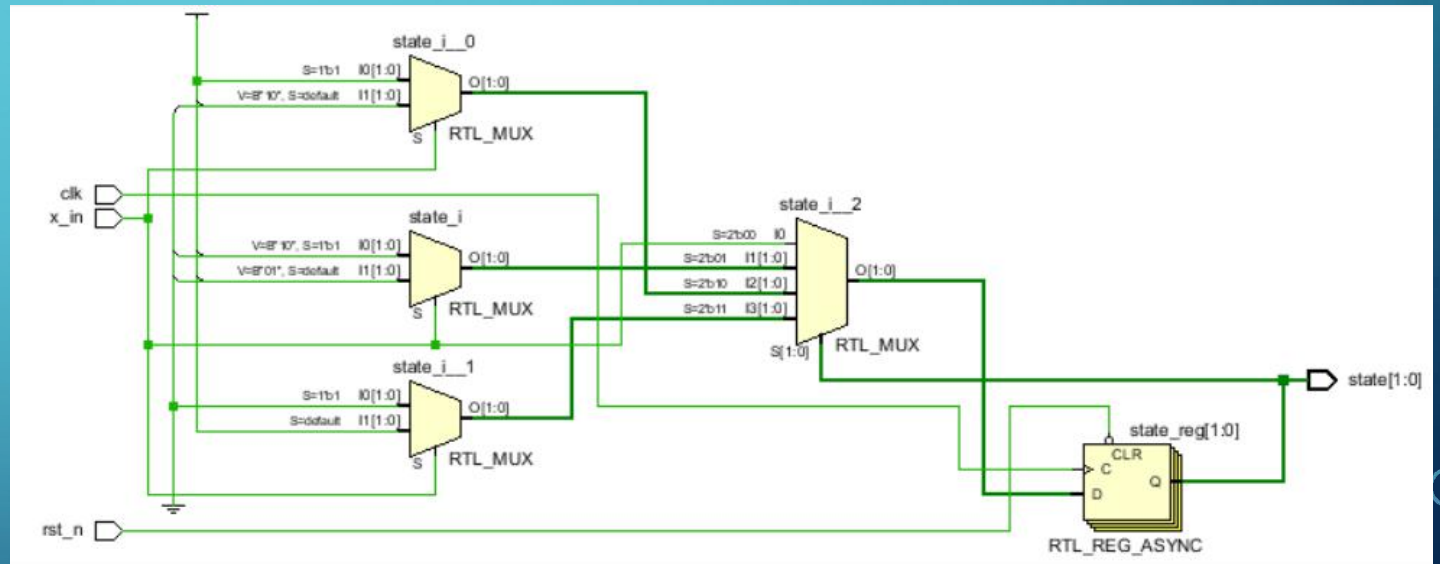

MOORE MODE WITH 2-STAGES

```
`timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
module moore_2b(input clk,rst_n,x_in,output[1:0] state,next_state);
  reg [1:0] state,next_state;
  parameter S0=2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
  always @(posedge clk,negedge rst_n) begin
    if(~rst_n
      state <= S0;
    else
      state <= next_state;
    end
  always @(state,x_in) begin
    case(state)
      S0: if(x_in) next_state = S1; else next_state = S0;
      S1: if(x_in) next_state = S2; else next_state = S1;
      S2: if(x_in) next_state = S3; else next_state = S2;
      S3: if(x_in) next_state = S0; else next_state = S3;
    endcase
  end
end
endmodule
```

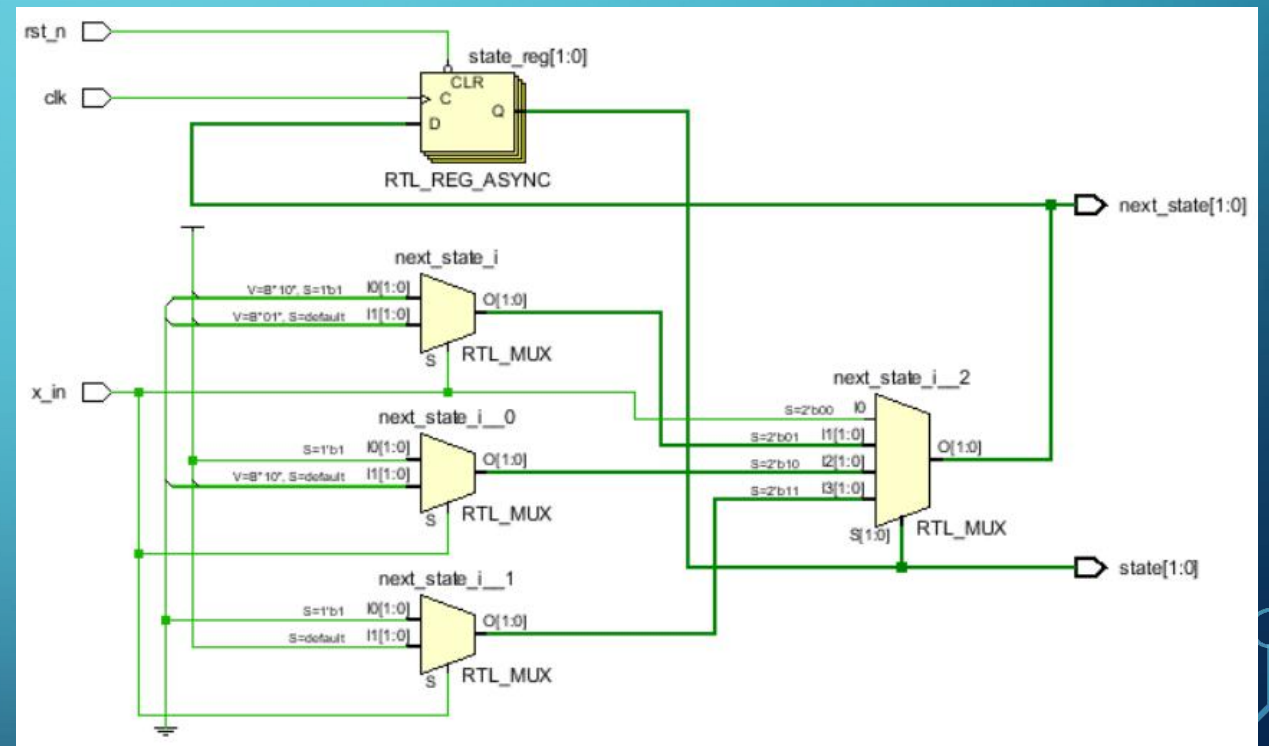


SIMULATION ON ONE & TWO STAGE OF MOORE

```

`timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////
module sim_moore_12();
reg clk,rst_n,x_in;
wire [1:0] u1s,u2s,u2ns;
moore_1b u1(clk,rst_n,x_in,u1s);
moore_2b u2(clk,rst_n,x_in,u2s,u2ns);
initial #70 $finish;
initial begin
clk = 1'b0;
rst_n=1'b0;
forever #5 clk=~clk;
end

 initial fork
    x_in=1'b0;
    #1 rst_n = 1'b1;
    #3 x_in = 1'b1;
    #35 x_in = 1'b0;
    #40 x_in = 1'b1;
join
endmodule
    
```



always
#5



always@(. . . . ,)/*
.....

always@(posedge , negedge)
.....

MEALY MODE

一段式不能使用

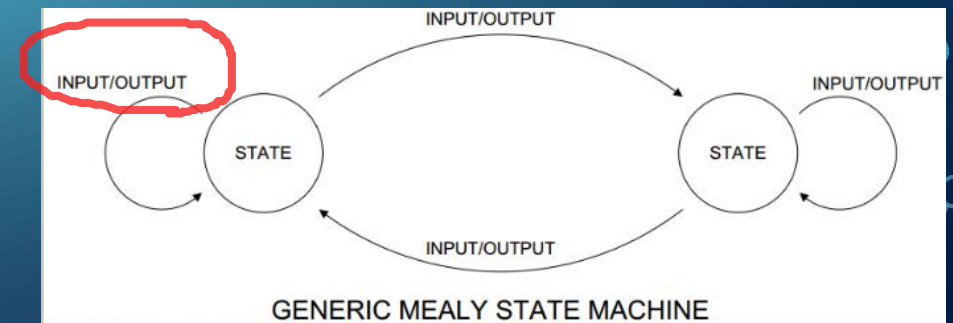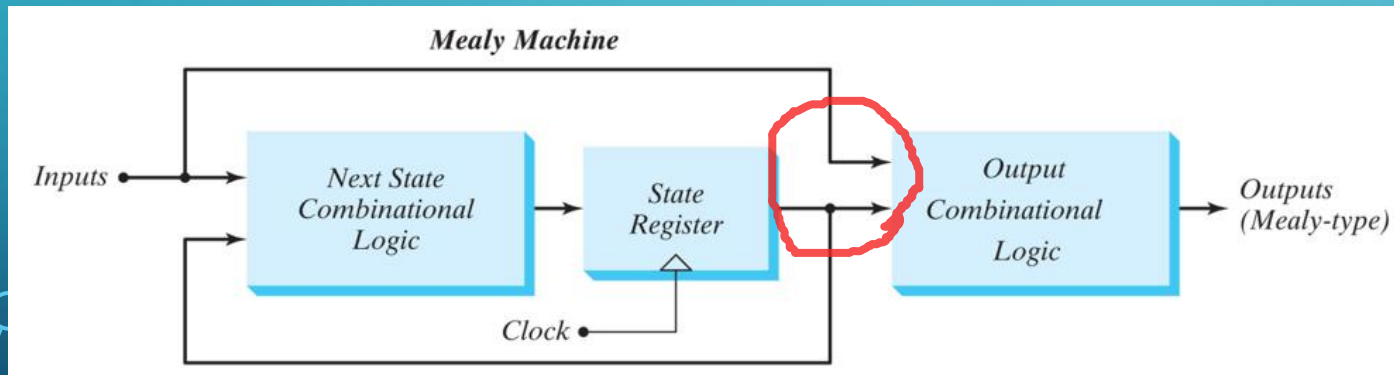- Outputs are functions of both present state and inputs
- Outputs may change if inputs change



MEALY MODE WITH 1-STAGE

不能在敏感列表中同时
加电频信号和时钟跳跃
沿

```
timescale 1ns / 1ps
////////////////////////////////////
module mealy_1b(input clk,rst_n,x_in,output[1:0] state,output y);
reg [1:0] state;
reg y;
parameter S0=2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
always @(posedge clk,negedge rst_n) begin
    if(~rst_n)
    begin
        state <= S0;
        y <= 1'b0;
    end
    else
    case(state)
    S0: if(x_in) {state,y} <= {S1,1'b0}; else {state,y} <= {S0,1'b0};
    S1: if(x_in) {state,y} <= {S2,1'b0}; else {state,y} <= {S1,1'b0};
    S2: if(x_in) {state,y} <= {S3,1'b0}; else {state,y} <= {S2,1'b0};
    S3: if(x_in) {state,y} <= {S0,1'b1}; else {state,y} <= {S3,1'b0};
    endcase
end
endmodule
```

MEALY MODE WITH TWO-STAGES

```
timescale 1ns / 1ps
/////////////////////////////////////////////////////////////////
module mealy_2b(input clk,rst_n,x_in,output[1:0] state,next_state,output y);
reg [1:0] state,next_state;
reg y;
parameter S0=2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
always @(posedge clk,negedge rst_n) begin
    if(~rst_n)
    begin
        state <= S0;
        y <= 1'b0;
    end
    else
        state <= next_state;
end
always @(state,x_in) begin
    case(state)
    S0: if(x_in) {next_state,y} = {S1,1'b0}; else {next_state,y} = {S0,1'b0};
    S1: if(x_in) {next_state,y} = {S2,1'b0}; else {next_state,y} = {S1,1'b0};
    S2: if(x_in) {next_state,y} = {S3,1'b0}; else {next_state,y} = {S2,1'b0};
    S3: if(x_in) {next_state,y} = {S0,1'b1}; else {next_state,y} = {S3,1'b0};
    endcase
end
endmodule
```

MEALY MODE WITH THREE-STAGES


```
module mealy_3b(input clk,rst_n,x_in,output[1:0] state,next_state,output y)
reg [1:0] state,next_state;
reg y;
parameter S0=2'b00,S1=2'b01,S2=2'b10,S3=2'b11;
always @(posedge clk,negedge rst_n) begin...
always @(state,x_in) begin...
always @(state,x_in) begin...
endmodule
```

```
always @(posedge clk,negedge rst_n) begin
    if(~rst_n)
    begin
        state <= S0;
        y <= 1'b0;
    end
    else
        state <= next_state;
end
```


```
always @(state,x_in) begin
    case(state)
    S0: if(x_in) next_state = S1; else next_state = S0;
    S1: if(x_in) next_state = S2; else next_state = S1;
    S2: if(x_in) next_state = S3; else next_state = S2;
    S3: if(x_in) next_state = S0; else next_state = S3;
    endcase
end
```

```
always @(state,x_in) begin
    case(state)
    S0,S1,S2: y=1'b0;
    S3: if(x_in) y=1'b1; else y=1'b0;
    endcase
end
```

SIMULATION RESULT

 

SCHEMATIC ON RTL VIEW

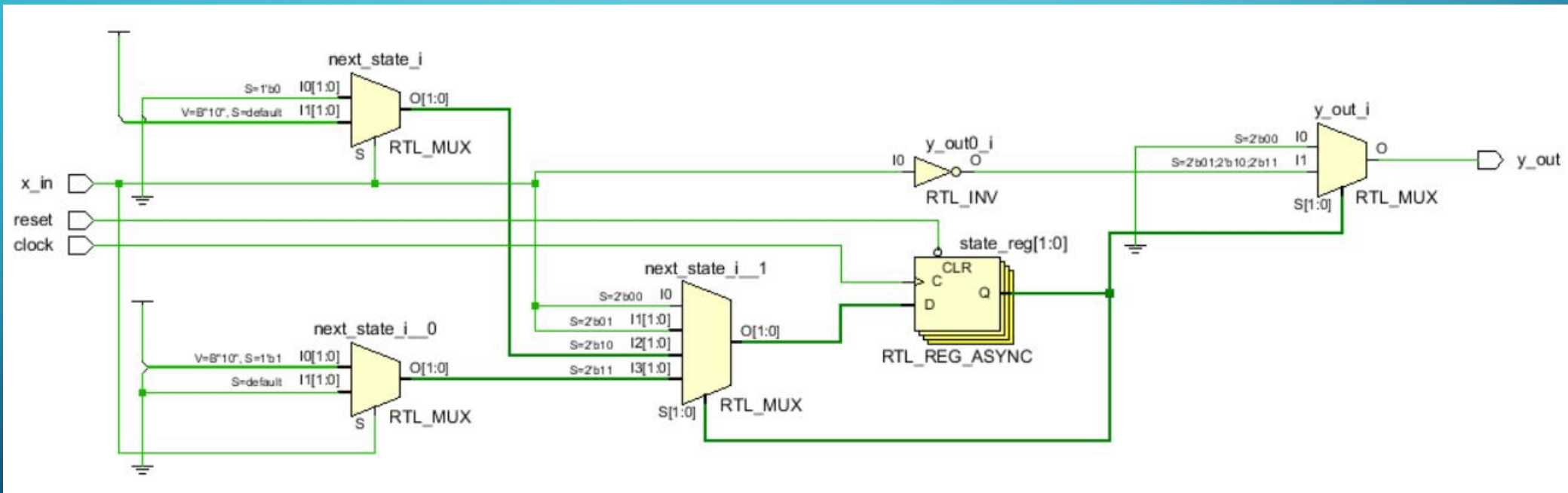

MOORE VS MEALY

- Moore mode :
 - output is the state of the circuit ,usually not simplified the state
 - Relatively simple
- Mealy mode :
 - output is not the state of the circuit, the state can be simplified
 - Relatively complex

PRACTICE1

A circuit has 2 inputs (x_in (5bit-width), clk) and 1 output(y_out). The circuit get the state of x_in at every posedge of clk , If the total number of received 1 is a multiple of 5, then y_out is valid, otherwise y_out is invalid.

1. Do the design by using behavior modeling in verilog. Is this a moore mode or mealy mode? Try to implement the circuit by two-stages and three-stages respectively.
2. Build testbench and verify the function on this sequential circuit.
3. Try to implement the circuit on Minisys board

PRACTICE2

A sequential circuit consists of three D flip-flops A , B and C, an input x_in .

while x_in : 0, the state of the circuit remains unchanged;

while x_in : 1, the state of the circuit passes through 001, 010, 100, and then back to 001, so the cycle.

1. Do the design by using behavior modeling in verilog. Is this a moore mode or mealy mode? Try to implement the circuit by two-stages.
2. Build testbench and verify the function on this sequential circuit.
3. Try to implement the circuit on Minisys board