



DIGITAL DESIGN

ASSIGNMENT 2

Deadline: 22:30, Wednesday 11 November 2019

Lab sessions & Location:

- 1. Lychee Garden 6, Room 406 (Wednesday 16:20-18:10 pm)**
- 2. Lychee Garden 6, Room 408 (Wednesday 19:00-20:50 pm)**
- 3. Lychee Garden 6, Room 402 (Thursday 8:00-9:50 am)**
- 4. Lychee Garden 6, Room 402 (Thursday 10:10~12:10 am)**

Teaching Assistant:

Wang Wei, email: wangw6@sustech.edu.cn

Hua Zheng Chang, email: huazc@mail.sustech.edu.cn

PART 1: DIGITAL DESIGN THEORY

Provide answers to the following questions:

1. Given the Boolean functions F1 and F2, show that
 - a. The Boolean function $E = F1 + F2$ contains the sum of the minterms of F1 and F2
 - b. The Boolean function $G = F1 \cdot F2$ contains only the minterms that are common to F1 and F2 .
2. Convert each of the following to the other canonical form.
 - a. $F(x, y, z) = \sum(1, 3, 7)$
 - b. $F(A, B, C, D) = \prod(1, 3, 5, 8, 11, 13, 15)$
3. Write the following Boolean expressions in:
 - a. $(b' + d)(a' + b' + c)(a + c)$ SOP form
 - b. $ab + a'c' + bc$ POS form
4. Determine whether the following Boolean equation is true or false. Show your process.
 - a. $y'z' + yz' + x'z = x'z'$
 - b. $x'y' + x'z' + yz = x'y + x'z$
5. Simplify the following Boolean functions and expressions, using four-variable maps:
 - a. $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$
 - b. $F(w, x, y, z) = \sum(1, 3, 4, 5, 6, 7, 9, 11, 13, 15)$
 - c. $A'BCD + ABC + CD + B'D$
 - d. $A'B'C'D' + BC'D + A'C'D + A'BCD + ACD$
6. Implement the following logical functions with two-level NOR gate circuits. Write down the simplification process, then draw the circuit diagram.
 - a. $F(A, B, C, D) = AD + BC'D + ABC + A'BC'D$
 - b. $F(A, B, C, D) = (A' + C' + D')(A' + C')(C' + D')$
7. Simplify the following Boolean function F, together with the don't-care conditions d, and then express the simplified function in sum-of-minterms form:
 - a. $F(x, y, z) = \sum(0, 1, 4, 5, 6)$ with $d(x, y, z) = \sum(2, 3, 7)$
 - b. $F(A, B, C, D) = \sum(5, 6, 7, 12, 14)$ with $d(x, y, z) = \sum(3, 9, 11)$

8. Implement the following Boolean expression with exclusive-OR and AND gates, draw the circuit diagram: $F = AB'CD' + A'BCD' + AB'C'D + A'BC'D$

PART 2: DIGITAL DESIGN LAB

INTRODUCTION

In this lab, you are required to use Vivado 2017.4 and Minisys Practice platform (xilinx FPGA chip artix 7 inside) to design a combinational logic circuit and test it.

PREAMBLE

Before working on the coursework itself, you should master the following material.

1. 'Ch2-Boolean Algebra-ICs-SUSTC.ppt' and 'CH3-Minimisation-SUSTC' in Sakai site.
2. 'Digital design lab5', 'Digital design lab6' and 'Digital design lab7' in Sakai site.
3. Verilog: <http://www.verilog.com>

EXERCISE SPECIFICATION

TASK1:

There are 16 wards, which are numbered from 0 to F respectively, among which the #0 ward has the lowest priority, and the #F has the highest priority (Priority increases as the number increases). Each room has a call bell, it can be turn on and turn off. In the main control room there is a 7-seg tube which shows the ID of the room whose bell is on with the highest priority.

Write a circuit to realize this function and test.

The circuit should get the info of wards whose call bell is on and light One 7-seg tube to show the ID of room whose bell is on with the highest priority.

- Do the design.
- Create the constraint file.

- Do the synthetic and implementation, generate the bitstream file and program the device, then test on the Minisys develop board.
- While Testing the circuit, at least three test scenarios need to be considered:
 - i. Only one ward's call bell is turned on
 - ii. Two or more wards whose call bell is turned on
 - iii. There is no ward whose call bell is turned on //NOTICE: This test scenarios should be distinguished from #0 ward's call bell is turned on.

TASK2:

Implement the circuit and test its function: $F(a,b,c,d) = a^a b^b c^c d^d$

- Write its true-table and K-map, using K-map to simplified the circuit if possible.
- Using data flow to Realization of circuit design in SOP and POS style respectively
- Write testbench in Verilog and do the simulation to verify the function of design

SUBMISSION

Submit your assignment report to the Sakai on *Corresponding site* "CS207-Prof.G" by the deadline.

ASSESSMENT

The full marks for this exercise is 100 and they are distributed as follows:

Theory: 40%

Question 1	4
Question 2	4
Question 3	4
Question 4	4

Question 5	8
Question 6	8
Question 7	4
Question 8	4
Total	40 marks

Lab: 60%

Task 1: Design in Verilog	5 marks
Task 1: Constrains file	5 marks
Task 1: photos about test result on Minisys practice board and description on inputs and outputs. 3 test at least	5*3 marks
Task 2: truth-table and K-map of the circuit	5*2 marks
Task 2: Design in Verilog in data flow style with SOP and POS in one module	5*2
Task 2: Test bench in Verilog, simulation result and its description	5*2 marks
Problem and solution. if there is no problem, suggestions or solutions is asked.	5 marks
Total	60 marks