



DIGITAL DESIGN

ASSIGNMENTREPORT

ASSIGNMENT ID : III

Student Name: 郑鑫颖

Student ID: 11912039

PART 1: DIGITAL DESIGN THEORY

Provide your answers here:

Digital Design Assignment III

1: $F(A, B, C, D) = \sum(1, 3, 5, 8, 9, 10, 11, 13, 15)$

AB \ CD	00	01	11	10
00	0	1	1	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

(a) AND-OR

$$F = C'D + AD + B'D + AB'$$

(b) OR-AND

$$F = (A+D) \cdot (B'+D) \cdot (A+B'+C')$$

(c) NOR-OR

$$F = (C+D')' + (A'+D')' + (B+D')' + (A'+B)'$$

(d) NOR-NOR

$$F = [(A+D)' + (B'+D)' + (A+B'+C')']'$$

(e) NAND-NAND

$$F = [(C'D)' \cdot (AD)' \cdot (B'D)' \cdot (AB')']'$$

(f) NAND-AND


$$F = (A'D)' \cdot (B'D)' \cdot (A'BC)'$$

2: parity generator

A	B	C	D	P
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$P = \sum(1, 2, 4, 7, 8, 11, 13, 14)$$

$$= A \oplus B \oplus C \oplus D$$

 

0	1	3	2
4	5	7	6
12	13	15	14
8	9	11	10




Parity Checker

A	B	C	P	Error-check
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

$$\text{Error-check} = \sum(1, 2, 4, 7, 8, 11, 13, 14)$$

$$= A \oplus B \oplus C \oplus P$$

 

0	1	3	2
4	5	7	6
12	13	15	14
8	9	11	10


3.

	input			output		
	X	Y	Z	A	B	C
0	0	0	0	0	0	1
1	0	0	1	0	1	0
2	0	1	0	0	1	1
3	0	1	1	1	0	0
4	1	0	0	0	1	1
5	1	0	1	1	0	0
6	1	1	0	1	0	1
7	1	1	1	1	1	0

$$A = \sum(3, 5, 6, 7) = XZ + XY + YZ$$

$$B = \sum(1, 2, 4, 7) = X \oplus Y \oplus Z$$

$$C = \sum(0, 2, 4, 6) = Z'$$

 

A B C



5. $F(A, B, C, D) = \Sigma(1, 2, 5, 8, 10, 14)$


(a)

	A	B	C	D	F	
0	0	0	0	0	0	D
1	0	0	0	1	1	
2	0	0	1	0	1	D'
3	0	0	1	1	0	
4	0	1	0	0	0	D
5	0	1	0	1	1	
6	0	1	1	0	0	0
7	0	1	1	1	0	
8	1	0	0	0	1	D'
9	1	0	0	1	0	
10	1	0	1	0	1	D'
11	1	0	1	1	0	
12	1	1	0	0	0	0
13	1	1	0	1	0	
14	1	1	1	0	1	D'
15	1	1	1	1	0	



(b)

	A	B	C	D	F	
0	0	0	0	0	1	
1	0	0	0	1	1	
2	0	0	1	0	1	
3	0	0	1	1	1	
4	0	1	0	0	0	0
5	0	1	0	1	0	
6	0	1	1	0	1	
7	0	1	1	1	1	
8	1	0	0	0	1	
9	1	0	0	1	1	
10	1	0	1	0	0	D'
11	1	0	1	1	0	
12	1	1	0	0	1	
13	1	1	0	1	1	
14	1	1	1	0	1	
15	1	1	1	1	1	


 


$$\begin{aligned}
 F &= A'B'C' + A'B'C + A'BC + AB'C' + AB'CD' \\
 &\quad + ABC' + ABC \\
 &= m_0x_1 + m_1x_1 + m_3x_1 + m_4x_1 + m_5x_1 \\
 &\quad + m_6x_1 + m_7x_1
 \end{aligned}$$

truth table

a (被减数)	b (减数)	C (低位借位)	X (本值)	Y (高位借位)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

For X:

  


PART 2: DIGITAL DESIGN LAB (TASK1)

DESIGN

Describe the design of your system by providing the following information:

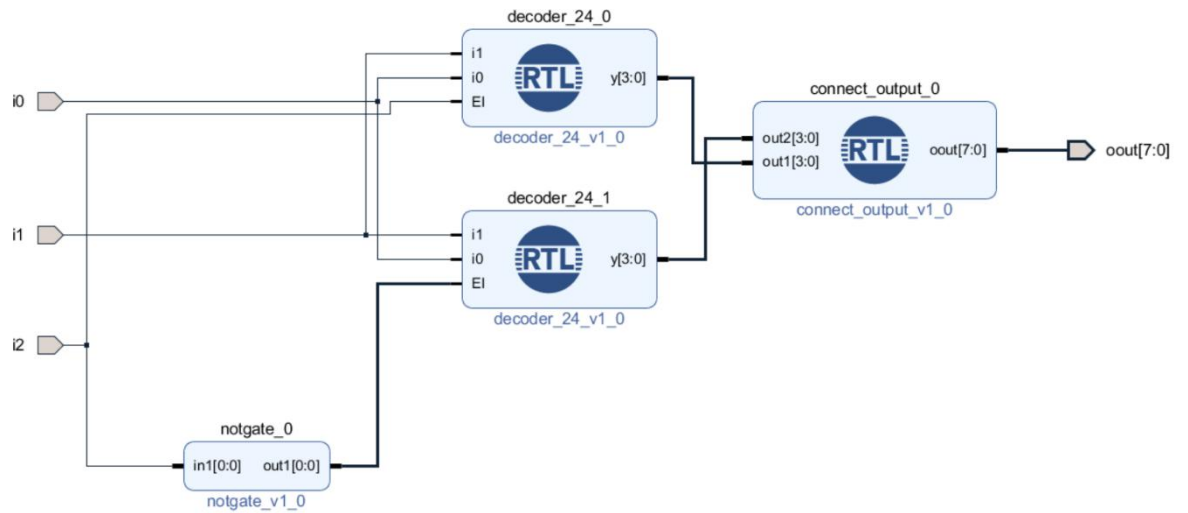3-8 decoder

- Verilog design (provide the Verilog code)



2-4 decoder

```

module decoder_24(
    input i1,
    input i0,
    input EI,
    output reg[3:0] y
);
always@*
begin
    if(~EI)
        casex({i1,i0})
            2'b00:y=4'b0001;
            2'b01:y=4'b0010;
            2'b10:y=4'b0100;
            2'b11:y=4'b1000;
        endcase
    else y=4'b0000;
    end
endmodule

```

• Truth-table for

i_2	i_1	i_0	$oout[7]$	$oout[6]$	$oout[5]$	$oout[4]$	$oout[3]$	$oout[2]$	$oout[1]$	$oout[0]$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0

0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

4-16 decoder

```

module decoder4_16(
    input i0,
    input i1,
    input i2,
    input i3,
    output reg [15:0] out
);

wire[15:0] out0;
decoder_38_wrapper v(i0, i1, i2, {out0[7], out0[6], out0[5], out0[4], out0[3], out0[2], out0[1], out0[0]});

always @* begin
    if(~i3)
        out={8'b0, out0[7], out0[6], out0[5], out0[4], out0[3], out0[2], out0[1], out0[0]};
    else
        out={out0[7], out0[6], out0[5], out0[4], out0[3], out0[2], out0[1], out0[0], 8'b0};
    end
endmodule

```

Truth-table for4-16

<i>I</i>	<i>I</i>	<i>I</i>	<i>I</i>	<i>Out0</i>	<i>Out0</i>	<i>Out0</i>	<i>Out0</i>	<i>Out0</i>	<i>Out0</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out</i>	<i>Out0</i>
<i>0₄</i>	<i>1₄</i>	<i>2₄</i>	<i>3₄</i>	<i>[15]₄</i>	<i>[14]₄</i>	<i>[13]₄</i>	<i>[12]₄</i>	<i>[11]₄</i>	<i>[10]₄</i>	<i>0[9]₄</i>	<i>0[8]₄</i>	<i>0[7]₄</i>	<i>0[6]₄</i>	<i>0[5]₄</i>	<i>0[4]₄</i>	<i>0[3]₄</i>	<i>0[2]₄</i>	<i>0[1]₄</i>	<i>0[0]₄</i>
<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>
<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>
<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>
<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>
<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>
<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>
<i>0₄</i>	<i>1₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>
<i>0₄</i>	<i>1₄</i>	<i>1₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>1₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>	<i>0₄</i>

1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

SIMULATION

Describe how you build the test bench and do the simulation.

- Using Verilog (provide the Verilog code)

3-8decoder

```

module decoder_sim();
    reg i0;
    reg i1;
    reg i2;
    wire[7:0] y;

    decoder_38_wrapper v(i0,
        i1,
        i2,
        y);
    /* decoder4_16 w(i0, i1, i2, i3, y); */

    initial begin
        {i0, i1, i2}=0;
        repeat(7) #10 {i0, i1, i2}={i0, i1, i2}+1;
        #10 $finish;
    end
endmodule

```

4-16decoder

```



module decoder_sim();
    reg i0;
    reg i1;
    reg i2;
    reg i3;
    wire[15:0] y;

    /*decoder_38_wrapper v(i0,
        i1,
        i2,
        y);*/
    decoder4_16 w(i0, i1, i2, i3, y);



    initial begin
        {i0, i1, i2, i3}=0;
        repeat(15) #10 {i0, i1, i2, i3}={i0, i1, i2, i3}+1;
        #10 $finish;
    end
endmodule

```

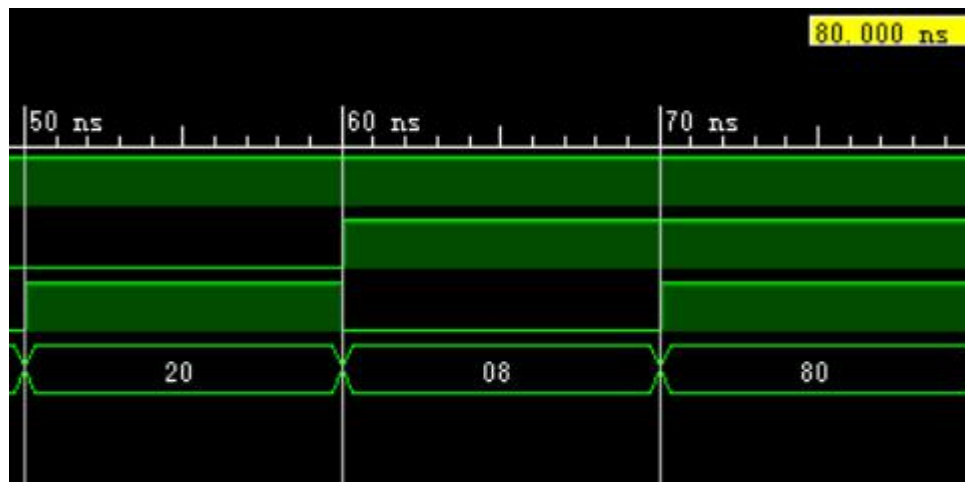 - Wave form of simulation result (provide screen shots)
- 3-8decoder



- 4-16decoder

  

- The description on whether the simulation result is same as the truth-table, is the function of the design meet the expectation.

the simulation result is same as the truth-table and meet the expectation

CONSTRAINT FILE AND THE TESTING

Describe how you test your design on the Minisys Practice platform.

- Constraint file (provide the screen shots on the feature of a pin and the binding info between pins and the input /output ports)

```
set_property IOSTANDARD LVCMOS33 [get_ports {i0}]
set_property IOSTANDARD LVCMOS33 [get_ports {i1}]
set_property IOSTANDARD LVCMOS33 [get_ports {i2}]
set_property IOSTANDARD LVCMOS33 [get_ports {i3}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[4]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[5]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[6]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[7]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[8]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[9]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[10]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[11]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[12]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[13]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[14]}]
set_property IOSTANDARD LVCMOS33 [get_ports {out[15]}]
set_property PACKAGE_PIN Y8 [get_ports {i0}]
set_property PACKAGE_PIN Y7 [get_ports {i1}]
set_property PACKAGE_PIN W9 [get_ports {i2}]
set_property PACKAGE_PIN Y9 [get_ports {i3}]
set_property PACKAGE_PIN A21 [get_ports {out[0]}]
set_property PACKAGE_PIN E22 [get_ports {out[1]}]
set_property PACKAGE_PIN D22 [get_ports {out[2]}]
```



```


set_property PACKAGE_PIN E21 [get_ports {out[3]]}
set_property PACKAGE_PIN D21 [get_ports {out[4]]}
set_property PACKAGE_PIN G21 [get_ports {out[5]]}
set_property PACKAGE_PIN G22 [get_ports {out[6]]}
set_property PACKAGE_PIN F21 [get_ports {out[7]]}
set_property PACKAGE_PIN J17 [get_ports {out[8]]}
set_property PACKAGE_PIN L14 [get_ports {out[9]]}
set_property PACKAGE_PIN L15 [get_ports {out[10]]}
set_property PACKAGE_PIN L16 [get_ports {out[11]]}
set_property PACKAGE_PIN K16 [get_ports {out[12]]}
set_property PACKAGE_PIN M15 [get_ports {out[13]]}
set_property PACKAGE_PIN M16 [get_ports {out[14]]}
set_property PACKAGE_PIN M17 [get_ports {out[15]]}

```

- The testing result (provide the screen shots (at least 3 testing scene) to show state of inputs and outputs along with the related descriptions.


15

0

 

3

7

 

THE DESCRIPTION OF OPERATION

Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.

- *Problems and solutions*

PART 2: DIGITAL DESIGN LAB (TASK2)

DESIGN

Describe the design of your system by providing the following information:

- *Verilog design while using data flow (provide the Verilog code)*

Design of 74151

```
module mutiplexer74151(  
    input EN,  
    input s2,  
    input s1,  
    input s0,  
    input d7,  
    input d6,  
    input d5,  
    input d4,  
    input d3,  
    input d2,  
    input d1,  
    input d0,  
    output reg y,  
    output w  
);  
always@*  
if(~EN)  
case({s2, s1, s0})  
    3'b000: y=d0;  
    3'b001: y=d1;  
    3'b010: y=d2;  
    3'b011: y=d3;  
    3'b100: y=d4;  
    3'b101: y=d5;  
    3'b110: y=d6;  
    3'b111: y=d7;  
endcase
```



```

        endcase
    else
        y=1'b0;

    assign w=~y;
endmodule

```

Truth table

EN	S2	S1	S0	y
0	0	0	0	d0
0	0	0	1	d1
0	0	1	0	d2
0	0	1	1	d3
0	1	0	0	d4
0	1	0	1	d5
0	1	1	0	d6
0	1	1	1	d7
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0

1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Function design

```

| module functions(input A, B, C, D, output y1, output y2);
  wire w;
  mutiplexer74151 u(1'b0, A, B, C, D, D, D, 1'b0, D, D, 1'b0, 1'b1, y1, w);

  assign y2=(~A&~B&~C&~D)|(B&~C&D)|(~A&~C&D)|(~A&B&C&D)|(A&C&D);

| endmodule

```

Truth-table

A	B	C	D	Y1	Y2
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0

0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	1	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	1

SIMULATION

Describe how you build the test bench and do the simulation.

- *Using Verilog (provide the Verilog code)*

```


module funsim();
  reg A, B, C, D;
  wire y1, y2;

  functions f(A, B, C, D, y1, y2):

  initial begin
    {A, B, C, D}=4'b0;
    repeat(15) #10 {A, B, C, D}={A, B, C, D}+1;
    #10 $finish;
  end
endmodule

```

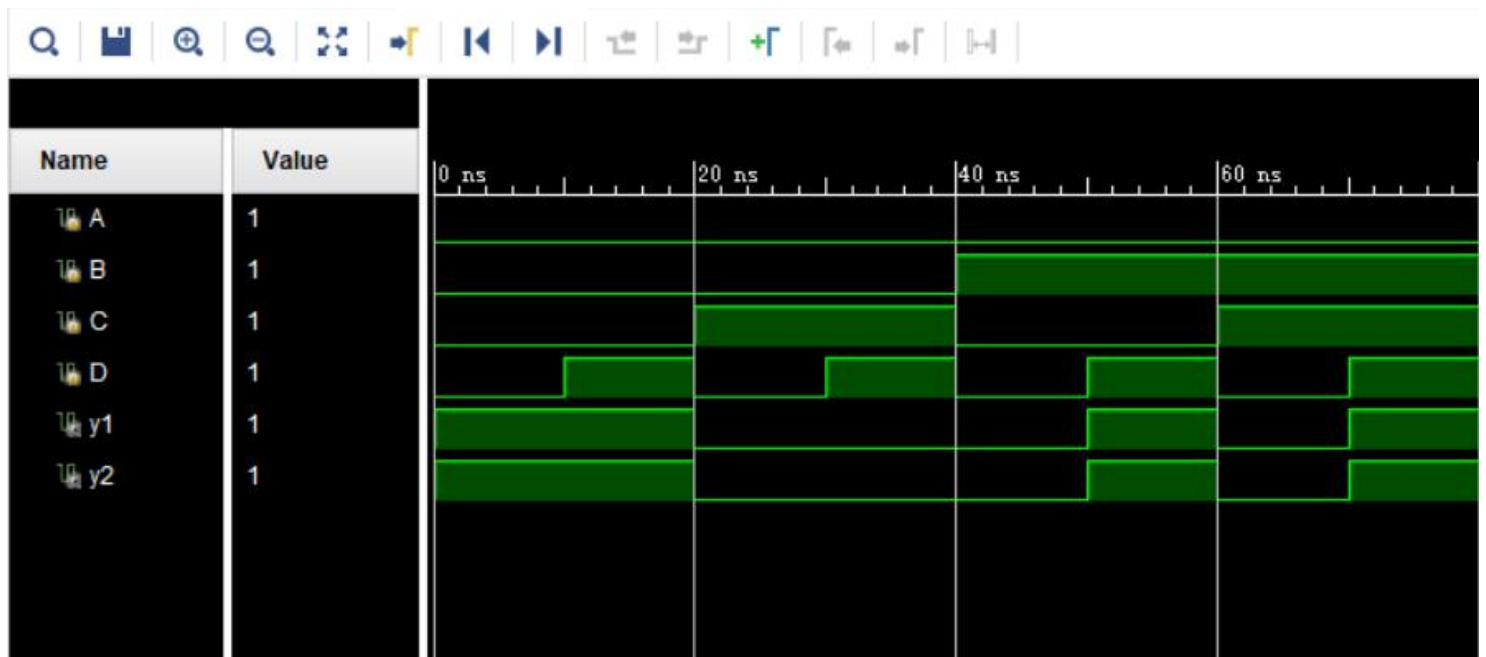- Wave form of simulation result (provide screen shots)



- The description on whether the simulation result is same as the truth-table, is the function of the design meet the expectation
the simulation result is same as the truth-table, the function of the design meet the expectation.



CONSTRAINT FILE AND THE TESTING


Describe how you test your design on the Minisys Practice platform.

- Constraint file (provide the screen shots on the feature of a pin and the binding info between pins and the input /output ports)

```
set_property IOSTANDARD LVCMOS33 [get_ports {A}]
set_property IOSTANDARD LVCMOS33 [get_ports {B}]
set_property IOSTANDARD LVCMOS33 [get_ports {C}]
set_property IOSTANDARD LVCMOS33 [get_ports {D}]
set_property IOSTANDARD LVCMOS33 [get_ports {y1}]
set_property IOSTANDARD LVCMOS33 [get_ports {y2}]
set_property PACKAGE_PIN Y9 [get_ports {A}]
set_property PACKAGE_PIN W9 [get_ports {B}]
set_property PACKAGE_PIN Y7 [get_ports {C}]
set_property PACKAGE_PIN Y8 [get_ports {D}]
set_property PACKAGE_PIN G22 [get_ports {y1}]
set_property PACKAGE_PIN F21 [get_ports {y2}]
```

  - The testing result (provide the screen shots (at least 3 testing scene)) to show state of inputs and outputs along with the related descriptions.



 

THE DESCRIPTION OF OPERATION

Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.

- *Problems and solutions*