

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue gradient background. The lines are vertical and horizontal, with some diagonal segments, and the circles are of varying sizes, resembling a circuit board or a digital network.

DIGITAL DESIGN

LAB10 SYNCHRONOUS SEQUENTIAL CIRCUIT


2020 FALL TERM @ CSE . SUSTECH

LAB10

- Synchronous sequential circuit
 - Latch 锁存器
 - Flip Flop (key point of lab10)
 - The conversion between each other
- Verilog
 - wire VS reg
- Practice

 4-2 PRIORITY-ENCODER IN LAB8


```
//4-2 priencoder
module encoder(
    input I0,
    input I1,
    input I2,
    input I3,
    output reg [1:0] Y
);
always @*
begin
    casex ({I3, I2, I1, I0})
        4'bxxx0: Y=2'b00;
        4'bxx01: Y=2'b01;
        4'bx011: Y=2'b10;
        4'b0111: Y=2'b11;
    endcase
end
endmodule
```



If there is no default and the case branch is incomplete, when the case branch is not listed in the case branch, the circuit state will remain unchanged, and then a latch will be generated to save the state.

LATCH

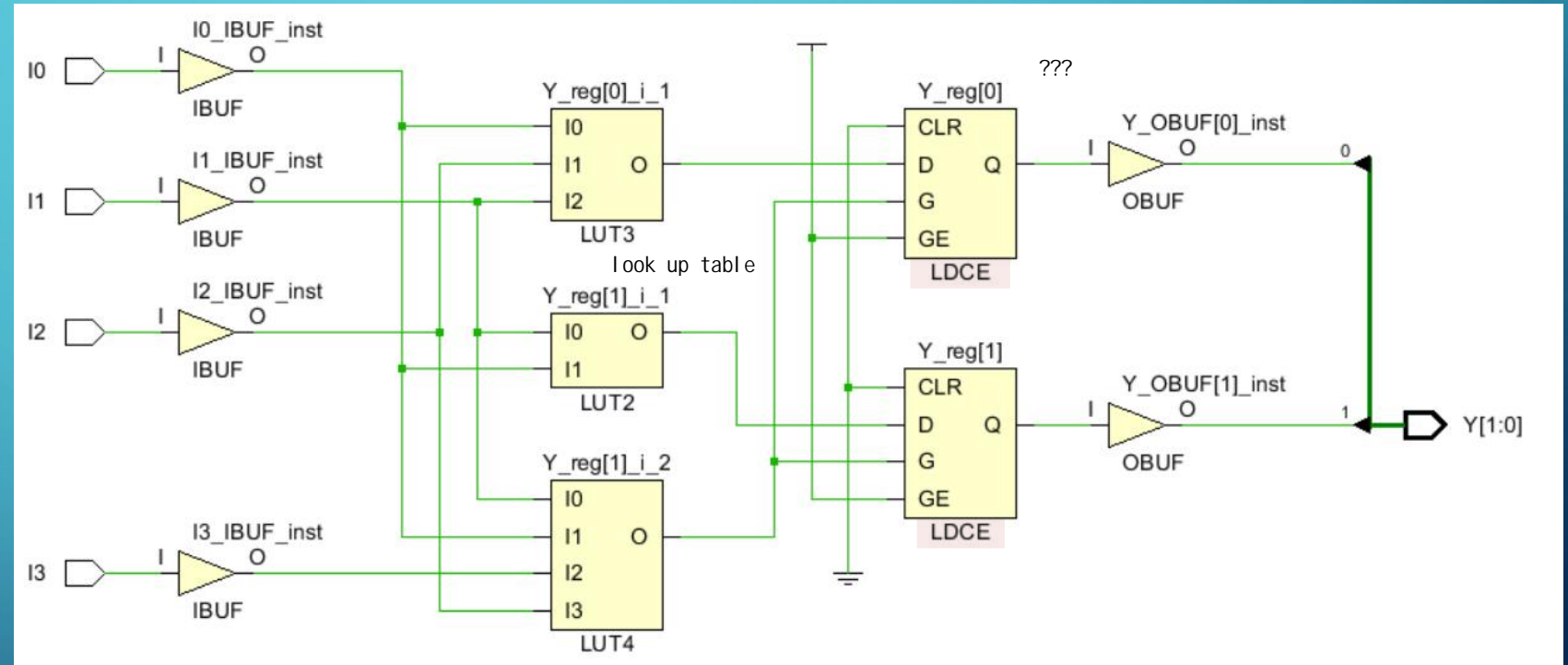
- The schematic of the synthesized design.
- LDCE: transparent Data Latch with Asynchronous Clear and Gate Enable



For more information on LDCE, please refer to *Xilinx 7 Series FPGA Libraries Guide for Schematic Design*

D LATCH

 - Latch: the simplest binary memory elements, static device composed of gates. When the input changes, the output changes immediately.



原语：输出在前面

reset 复位信号
set 置位信号



```
module D_Latch(  
    input En, D,  
    output reg Q,  
    output Qn  
);  
    assign Qn = ~Q;  
    always @*  
        if (En)  
            begin  
                Q = D;  
            end  
        else  
            Q = Q;  
    endmodule
```

D LATCH

- Schematic of RTL analysis:

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

非门对不定态取反还是不定态
与门：不定态与0会得到0

 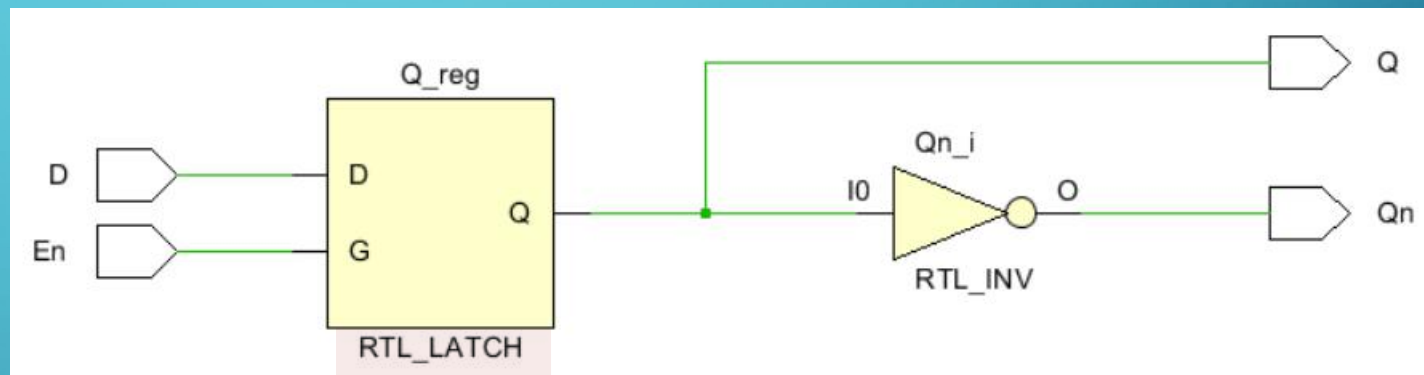

FLIP FLOP

- The storage elements (memory) used in clocked sequential circuits are called flipflops.
- The most economical and efficient flip-flop constructed is the edge-triggered D flipflop, because it requires the smallest number of gates.

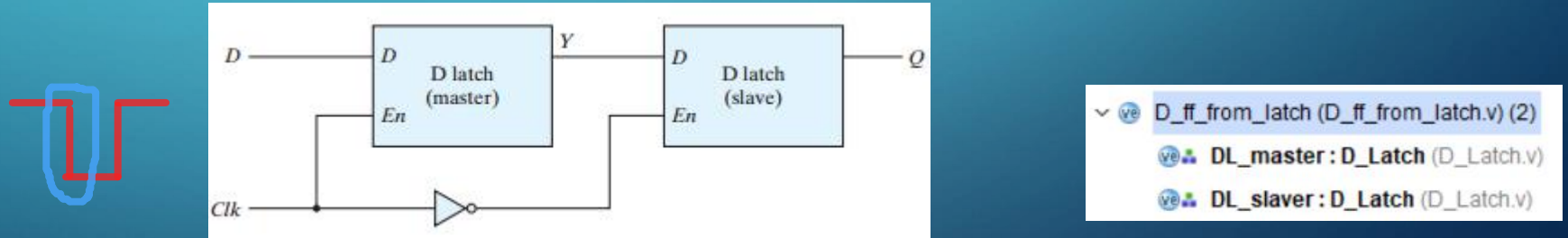


Figure for master-slave negative-edge triggered D flip-flop

D FLIP FLOP

$$Q^{n+1} = D$$


数据流：assign wire无法保存信号 无法敏感与跳跃沿

结构化建模

行为级建模：always

```
module D_flipflop(
input clk,D,
output reg Q,
output Qn
);
    always @(posedge clk)
    begin
        Q <= D; 非阻塞
    end
    assign Qn = ~Q;
endmodule
```

Clk	Q
↑	D
0	no change
1	no change
↓	no change

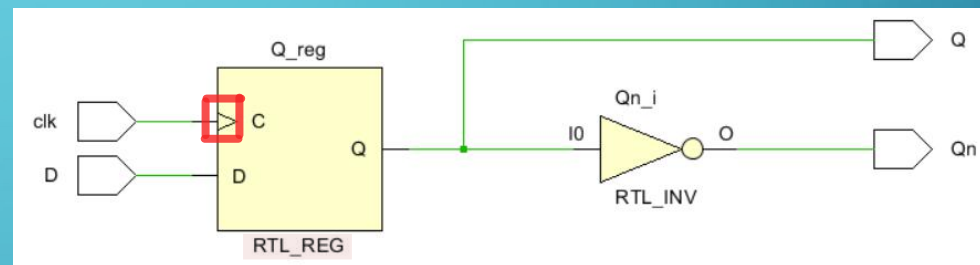

```
scl k=1' b0;
forever #5 scl k=~scl k
```


JK FLIP FLOP(1)


- $Q^{n+1} = J\bar{Q}^n + \bar{K}Q^n$

J	K	Q^{n+1}
0	0	no change
0	1	<u>0</u>
1	0	<u>1</u>
1	1	Q^n'

reset

set

JK Q^n	00		01		11		10	
	0	1	0	1	0	1	0	1
0	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	1	0

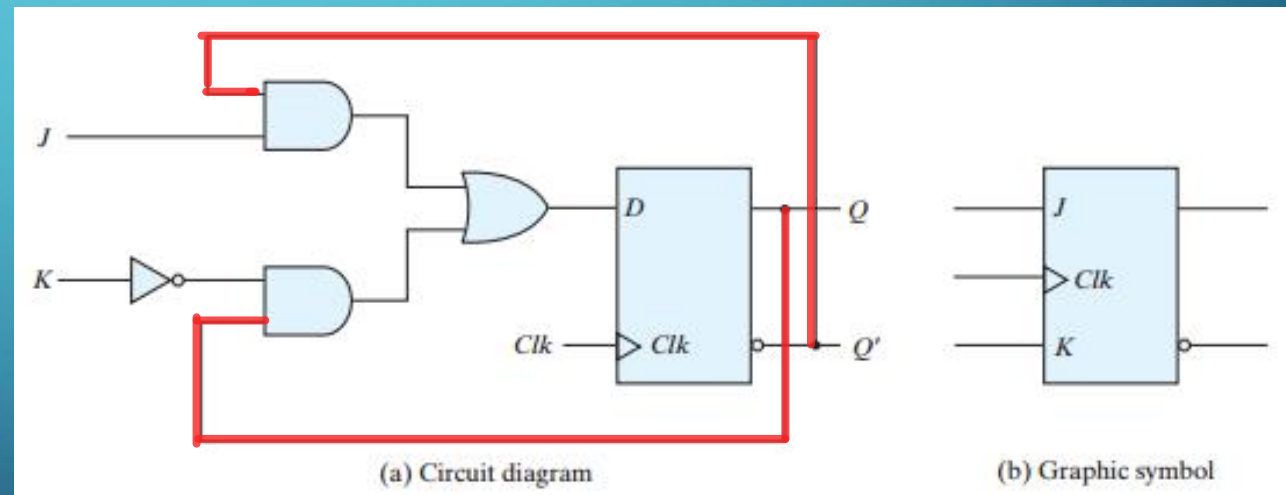

JK FLIP FLOP(2)

$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$


```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q,  
    output Qn  
);  
    assign Qn = ~Q;  
    always @(posedge Clk)  
    if({J, K} == 2'b10) //set  
    begin  
        Q <= 1'b1;  
    end  
    else if ({J, K} == 2'b01) //reset  
    begin  
        Q <= 1'b0;  
    end  
    else if ({J, K} == 2'b11) //reverse  
    begin  
        Q <= Qn;  
    end  
end  
endmodule
```



USING JK FLIP FLOP TO IMPLEMENT D FLIP FLOP

- JK Flip-Flop: $Q^{n+1} = \underline{J}\overline{Q}^n + \underline{K}Q^n$
- D Flip-Flop: $Q^{n+1} = D = \underline{D}\overline{Q}^n + \underline{D}Q^n$
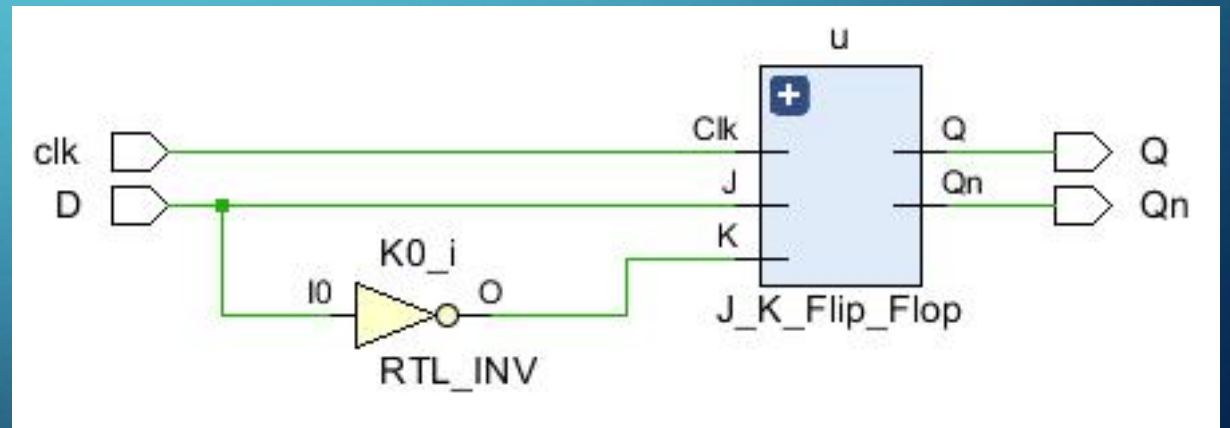
```
module D_Flip_Flop_JK(  
    input clk, D,  
    output Q, Qn  
);  
    J_K_Flip_Flop u(clk, D, ~D, Q, Qn);  
endmodule
```





T FLIP FLOP

- The T (toggle) flip-flop is a complementing flip-flop, which can be obtained from a JK flip-flop when inputs J and K are tied together.

T	Q^{n+1}
0	Q^n
1	$\sim Q^n$

```
module T_Flip_Flop(  
    input Clk, T,  
    output reg Q,  
    output Qn  
);  
    assign Qn = ~Q;  
    always @(posedge Clk)  
        case (T)  
            1'b1: Q <= Qn;  
        endcase  
endmodule
```
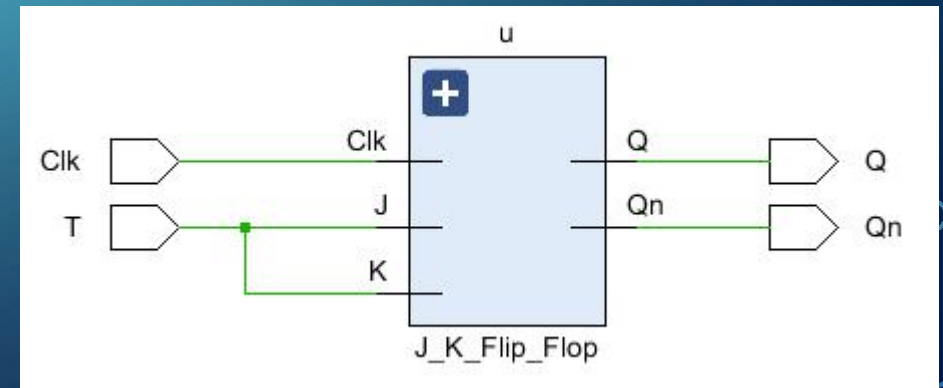 
```
module T_Flip_Flop_JK(  
    input T, Clk,  
    output Q,  
    output Qn  
);  
    J_K_Flip_Flop u(Clk, T, T, Q, Qn);  
endmodule
```




WIRE VS REG(1)

- There are two data types in Verilog: **wire** and **register**.
 - **wire** is a kind of net, which is equivalent to physical connection.
 - **wire** is used to connect two points, and thus does **not have any driving strength**.
 - **wire** data types can be used for connecting the output port to the actual driver.
 - a **wire** can be assigned a value by a continuous assign statement, which is used for designing **combinational logic**.
 - **default data type is wire**: this means that if you declare a port or variable without specifying reg or wire, it will be a 1-bit wide wire.
 - **reg** is a kind of register, which is equivalent to memory cell.
 - reg can **store value and drive strength**. Reg can be used for **modeling both combinational and sequential logic**.
 - **reg** data type can be driven from initial and always block.
 - The LHS of a behavioral block(initial , always) should be declared as **reg**

WIRE VS REG(2)

 - input port could drive by both wire/register, but it could only be declared as wire
- **output port** can be declared as wire or register, but it can only drive wire
- bidirectional port can only be declared as wire



PRACTICE(1)

- Try to construct a T Flip Flop with gates.
 - Do the design and verify the function of your design.
 - Create the constraint file, do the synthesis and implementation, generate the bitstream file and program the device, then test on the minisys develop board.

复位信号

PRACTICES(2)


$$Q^{n+1} = J\overline{Q}^n + \overline{K}Q^n$$

- Can this JK flip-flop work?
- Try to use it implement a T flip-flop, do the design, create constraint file, generate the bitstream file and program the device.
- Can the T flip-flop work? Explain the reason.

```
module J_K_Flip_Flop(  
    input Clk, J, K,  
    output reg Q, Qn  
);  
    always @(posedge Clk)  
        if({J, K} == 2'b10) //set  
            begin  
                {Q, Qn} <= 2'b10;  
            end  
        else if ({J, K} == 2'b01) //reset  
            begin  
                {Q, Qn} = 2'b01;  
            end  
        else if ({J, K} == 2'b11) //reverse  
            begin  
                Q <= Qn;  
                Qn <= Q;  
            end  
    end  
endmodule
```

TIPS:

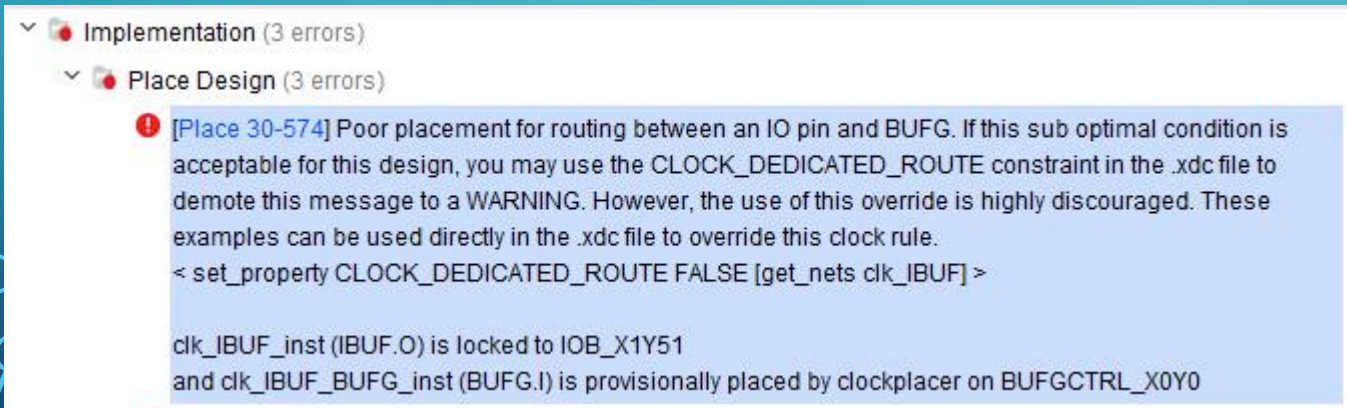- Constraints: if you want to use IO pin as clock, you should use the CLOCK_DEDICATED_ROUTE constraint in the .xdc file to demote the Error message to a WARNING.



```
set_property PACKAGE_PIN Y9 [get_ports clk]
set_property PACKAGE_PIN W9 [get_ports D]
set_property PACKAGE_PIN K17 [get_ports Q]
set_property PACKAGE_PIN L13 [get_ports Qn]
set_property IOSTANDARD LVCMOS33 [get_ports clk]
set_property IOSTANDARD LVCMOS33 [get_ports D]
set_property IOSTANDARD LVCMOS33 [get_ports Q]
set_property IOSTANDARD LVCMOS33 [get_ports Qn]
set_property CLOCK_DEDICATED_ROUTE FALSE [get_nets clk_IBUF]
```