

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue gradient background. The lines and circles resemble a circuit board or a tree structure, with some lines ending in small circles.

# DIGITAL DESIGN

LAB12 FREQUENCY DIVIDER

2020 FALL TERM @ CSE . SUSTECH

# LAB12

- Frequency divider
  - Divide by even
  - Divide by odd
- Structure design
  - demo
    - Flowing light
    - 7-seg tube

# CLOCK ON MINISYS BOARD

10纳秒

- **Minisys** board includes a 100MHz crystal oscillator connected to the main chip Y18 pin. Through requirement design, the input clock can drive MMCMs or PLLs to produce multi-frequency clock and phase changes.

# FREQUENCY DIVIDER

- A **Frequency Divider**, also called a **clock divider** or scaler or pre-scaler, is a circuit that takes an input signal of a frequency  $f_{in}$ , and generates an output signal of a frequency  $f_{out}$ :

$$f_{out} = f_{in}/n \text{ (n is an integer).}$$

- For power-of-2 integer division, a simple binary counter can be used, clocked by the input signal. The least-significant output bit alternates at  $1/2$  the rate of the input clock, the next bit at  $1/4$  the rate, the third bit at  $1/8$  the rate, etc.
- An arrangement of flipflops is a classic method for integer-n division. Such division is frequency and phase coherent to the source over environmental variations including temperature. The easiest configuration is a series where each flip-flop is a divide-by-2. For a series of three of these, such system would be a divide-by-8. By adding additional logic gates to the chain of flip flops, other division ratios can be obtained. Integrated circuit logic families can provide a single chip solution for some common division ratios.

# FREQUENCY DIVIDER(N:4)

```
timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////
module clk_div(input clk,rst_n,output reg clk_out);
    parameter period = 4;
    reg [3:0] cnt;
    always@(posedge clk, negedge rst_n)
    begin
        if(~rst_n)begin
            cnt <=0;
            clk_out<=0;
        end
        else
            if(cnt==((period>>1) - 1)) begin
                clk_out <= ~clk_out;
                cnt <=0;
            end
            else begin
                cnt <= cnt+1;
            end
        end
    end
endmodule
```

异步复位信号

半周期计时一次

```
timescale 1ns / 1ps
////////////////////////////////////////////////////////////////////////////////
module clk_div_tb( );
    reg clk,rst_n;
    wire clk_out;
    clk_div cd(clk,rst_n,clk_out);
    initial fork
        clk <=0;
        rst_n <=0;
        # 3 rst_n <= 1;
        forever
            #5 clk = ~clk;
    join
endmodule
```

fork join 不能综合

占空比：一个时钟周期里  
高电平占比





# FREQUENCY DIVIDER(N:5)

```

timescale 1ns / 1ps
module clock_div(input clk,rst_n,output reg clk_out );
//reg [25:0]cnt:...
reg [2:0] step1,step2;
always@(posedge clk)begin
    if(~rst_n)begin
        step1<=3'b000;
    end
    else begin
        case(step1)
            3'b000: step1<=3'b001;
            3'b001: step1<=3'b011;
            3'b011: step1<=3'b100;
            3'b100: step1<=3'b010;
            3'b010: step1<=3'b000;
            default:step1<=3'b000;
        endcase
    end
end
end

```

```
assign clk_out=step1[0]|step2[0];
```

```

always @(negedge clk,negedge rst_n)
    if(~rst_n)
        step2<=3'b000;
    else
        case(step2)
            3'b000: step2<=3'b001;
            3'b001: step2<=3'b011;
            3'b011: step2<=3'b100;
            3'b100: step2<=3'b010;
            3'b010: step2<=3'b000;
            default:step2<=3'b000;
        endcase
    end
endmodule

```

```

timescale 1ns / 1ps
////////////////////////////////////

module clock_div_tb( );
reg clk,rst_n;
wire clk_out;
clock_div cd(clk,rst_n,clk_out);
initial fork
    clk <=0;
    rst_n <=0;
    # 3 rst_n <= 1;
    forever
        #5 clk = ~clk;
join
endmodule


```


 
# DEMO1 (FLOWING LIGHT1)

```
`timescale 1ns / 1ps
module flowing_light_lite(input clk,rst_n,output[7:0] led);
    reg [7:0] light_reg;
    always@(posedge clk,negedge rst_n)
    begin
        if(!rst_n)
            light_reg<=8'b0000_0001;
        else if(light_reg == 8'b1000_0000)
            light_reg<=8'b0000_0001;
        else
            light_reg<=light_reg<<1;
    end
    assign led = light_reg;
endmodule
```

```
`timescale 1ns / 1ps
module flow_water_tb( );
    reg clk,rst_n;
    wire [7:0]led;
    //flow_water_lights fs(clk,rst_n,led,cnt,ns);
    flowing_light_lite fs(clk,rst_n,led);
    initial fork
        rst_n <=1'b0;
        clk <= 1'b0;
        #2 rst_n <=1'b1;
        forever
            #5 clk = ~clk;
    join
endmodule
```



用拨码开关模拟时钟要加上一句话

# DEMO1 (FLOWING LIGHT2)

Minisys board includes a 100MHz crystal oscillator connected to the main chip Y18 pin.

```
`timescale 1ns / 1ps
module flash_led_top(
    input clk,
    input rst_n,
    input sw0,
    output [7:0]led
);


wire clk_bps;
counter counter(
    .clk( clk ),
    .rst_n( rst_n ),
    .clk_bps( clk_bps )
);
flash_led_ctl flash_led_ctl(
    .clk( clk ),
    .rst_n( rst_n ),
    .dir( sw0 ),
    .clk_bps( clk_bps ),
    .led( led )
);
endmodule
```

```
`timescale 1ns / 1ps
module counter(
    input clk,
    input rst,
    output clk_bps
);
    两级计数
    reg [13:0]cnt_first,cnt_second;
    always @( posedge clk or posedge rst )
        if( rst )
            cnt_first <= 14'd0;
        else if( cnt_first == 14'd10000 )
            cnt_first <= 14'd0;
        else
            cnt_first <= cnt_first + 1'b1;
    always @( posedge clk or posedge rst )
        if( rst )
            cnt_second <= 14'd0;
        else if( cnt_second == 14'd10000 )
            cnt_second <= 14'd0;
        else if( cnt_first == 14'd10000 )
            cnt_second <= cnt_second + 1'b1;
    assign clk_bps = cnt_second == 14'd10000 ? 1'b1 : 1'b0;
endmodule
```

```
module flash_led_ctl(
    input clk,
    input rst_n,
    input dir,
    input clk_bps,
    output reg[7:0]led
);
    always @( posedge clk or negedge rst_n )
        if( !rst_n )
            led <= 8'h80;
        else
            case( dir )
                1'b0: //从左向右
                    if( clk_bps )
                        if( led != 8'd1 )
                            led <= led >> 1'b1;
                        else
                            led <= 8'h80;
                1'b1: //从右向左
                    if( clk_bps )
                        if( led != 8'h80 )
                            led <= led << 1'b1;
                        else
                            led <= 8'd1;
            endcase
endmodule
```



# DEMO1 (FLOWING LIGHT2)

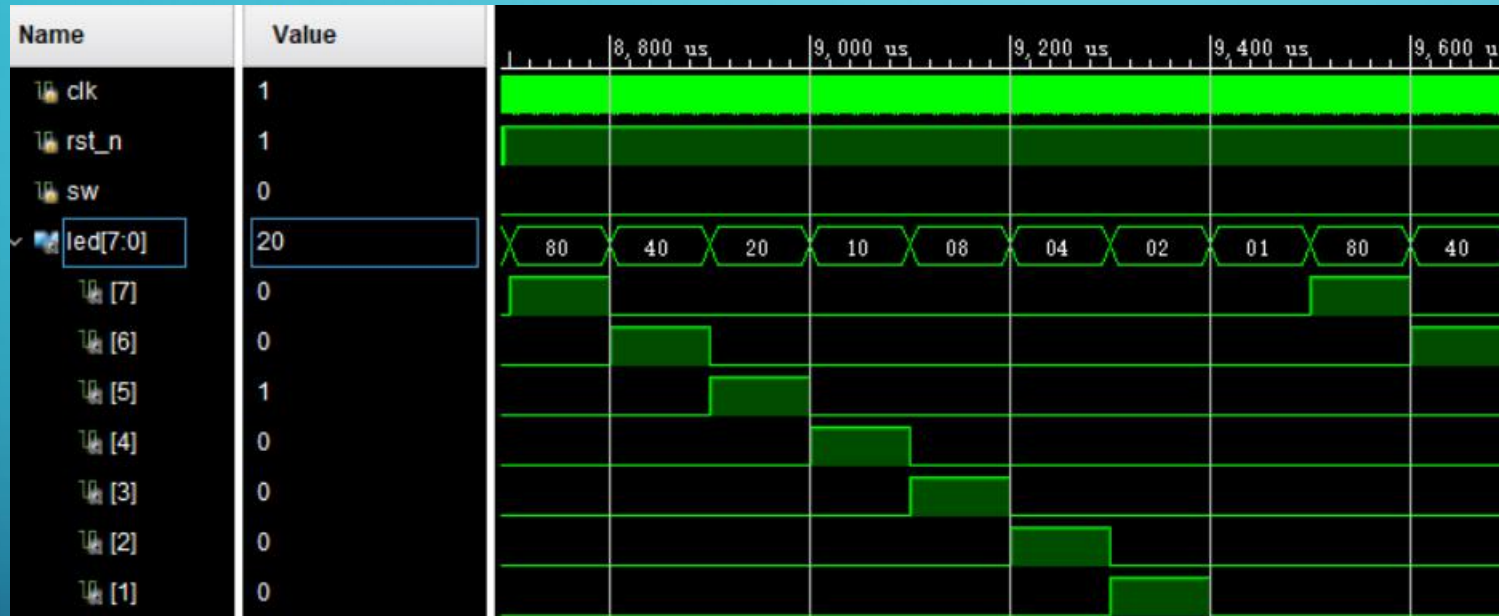

Test on Minisys board



```
set_property PACKAGE_PIN Y18 [get_ports clk]
```

# DEMO2 : 7-SEG TUBE



```
always @( posedge clk or negedge rst)  //frequency division : clk->clkout...

always @(posedge clkout or negedge rst) //change scan_cnt based on clkout    ...

always @( scan_cnt)                  //select tube...

always @ (scan_cnt ) //decoder to display on 7-seg tube...
```

异步复位 复位不受时钟信号控制 随时都可以复位

```
module scan_seg ( rst ,clk ,DIG ,Y );
    input rst ;//reset
    input clk ;//system clock 100MHz
    output [7:0] DIG ;//bit selection
    output [7:0] Y ;// seg selection

    reg clkout ; //
    reg [31:0] cnt;
    reg [2:0] scan_cnt ;

    parameter period= 200000;//500HZ stable
    //parameter period= 250000;//400HZ stable
    //parameter period= 5000000;//20HZ loop one by one
    //parameter period= 2500000;//40HZ twinkle
    //parameter period= 1000000;//100HZ twinkle

    reg [6:0] Y_r;
    reg [7:0] DIG_r;
    assign Y = {1'b1, (~Y_r[6:0])};//dot never light
    assign DIG = ~DIG_r;
```

# DEMO2 : 7-SEG TUBE

```
always @(posedge clk or negedge rst) //frequency division : clk->clkout
begin
    if (!rst) begin
        cnt <= 0;
        clkout <=0;
    end
    else begin
        if (cnt == (period >> 1) - 1)
            begin
                clkout <= ~clkout;
                cnt<=0;
            end
        else
            cnt<= cnt+1;
        end
    end
end
```

```
always @( scan_cnt) //select tube
begin
    case ( scan_cnt )
        3'b000 : DIG_r = 8'b0000_0001;
        3'b001 : DIG_r = 8'b0000_0010;
        3'b010 : DIG_r = 8'b0000_0100;
        3'b011 : DIG_r = 8'b0000_1000;
        3'b100 : DIG_r = 8'b0001_0000;
        3'b101 : DIG_r = 8'b0010_0000;
        3'b110 : DIG_r = 8'b0100_0000;
        3'b111 : DIG_r = 8'b1000_0000;
        default :DIG_r = 8'b0000_0000;
    endcase
end
```

```
always @(posedge clkout or negedge rst) //change scan_cnt based on clkout
begin
    if (!rst)
        scan_cnt <= 0 ;
    else begin
        scan_cnt <= scan_cnt + 1;
        if(scan_cnt==3'd7) scan_cnt <= 0;
    end
end
```

摩尔模式

```
always @ (scan_cnt ) //decoder to display on 7-seg tube
begin
    case (scan_cnt)
        0: Y_r = 7'b0111111; // 0
        1: Y_r = 7'b0000110; // 1
        2: Y_r = 7'b1011011; // 2
        3: Y_r = 7'b1001111; // 3
        4: Y_r = 7'b1100110; // 4
        5: Y_r = 7'b1101101; // 5
        6: Y_r = 7'b1111101; // 6
        7: Y_r = 7'b0100111; // 7
        8: Y_r = 7'b1111111; // 8
        9: Y_r = 7'b1100111; // 9
        10: Y_r = 7'b1110111; // A
        11: Y_r = 7'b1111100; // b
        12: Y_r = 7'b0111001; // c
        13: Y_r = 7'b1011110; // d
        14: Y_r = 7'b1111001; // E
        15: Y_r = 7'b1110001; // F
        default: Y_r = 7'b0000000;
    endcase
end
```

# PRACTICE

- 1. Implement a 'Breathing lamp' on Minsys board, the 'Breathing lamp' here is a led which light on for 1 seconds while light off for 1 seconds.
- 2. implement a Rolling subtitles showing 'CSE' and flowing from right to left on the tube of Minisys board.



# TIPS

If you have any problem about frequency divider, wish this demo will help you.  
2-stages is an easier way for understanding sequential circuit compared to 1-stage.

```
module clk_div_2(input clk,rst_n,output reg clk_out );  
  
    parameter period=4;  
    reg [3:0] cnt;  
    reg [3:0] cnt_ns;  
    reg clk_out_ns;  
    always@(posedge clk,negedge rst_n)...  
  
    always@(*)begin...  
  
    always@(posedge clk,negedge rst_n)...  
  
    always@(*)...  
endmodule
```

```
always@(posedge clk,negedge rst_n)  
begin  
    if(~rst_n)begin...  
    else  
        clk_out<=clk_out_ns;  
    end  
  
    always@(*)begin  
    if(~rst_n)  
        clk_out_ns = 1;  
    else  
        if(cnt==((period>>1)-1))  
            clk_out_ns = ~clk_out;  
        else  
            clk_out_ns = clk_out;  
        end  
    end
```

```
always@(posedge clk,negedge rst_n)  
begin  
    if(~rst_n)begin  
        cnt<=0;  
    end  
    else begin  
        cnt<=cnt_ns;  
    end  
end  
  
always@(*)  
begin  
    if(cnt==((period>>1)-1))  
        cnt_ns=0;  
    else  
        cnt_ns=cnt+1;  
    end
```

